

Lab - Assignment - 06

Name : Imam Hossain

ID : 18301276

Section: 07

Report:

1)

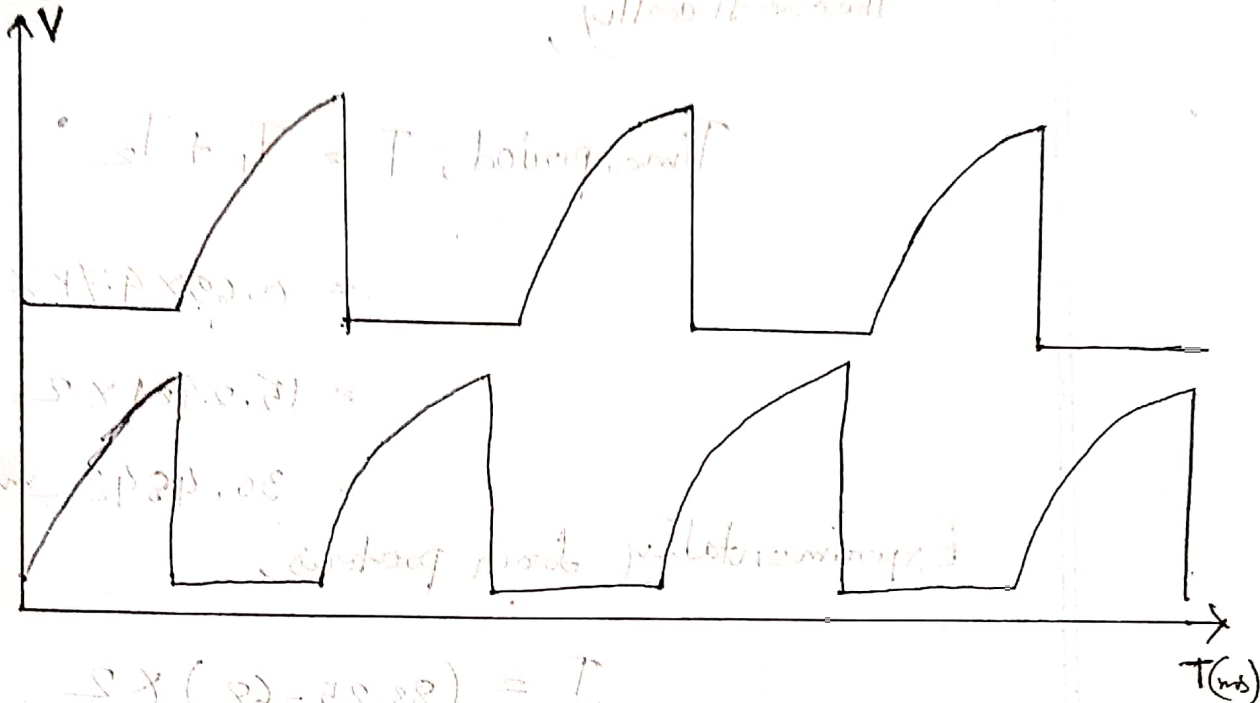


Fig: Output Waveforms

2) Yes, there is a deviation in the experimental output wave shape from the desired wave. We can see that experimental highest peak and lowest peak differs from theoretical values because we did not consider circuits' internal voltage drop.

3) Theoretically,

$$\text{Time period, } T = T_1 + T_2$$

$$= 0.69 \times 4.7K \times 4.7\mu F \times 2$$

$$= 15.2421 \times 2$$

$$= 30.4842 \text{ ms}$$

Experimentally from posters,

$$T = (83.25 - 68) \times 2$$

$$= 15.25 \times 2$$

$$= 30.5$$

So, both time periods are almost similar.

4) Yes, it is possible to use the multivibrator to create a variable frequency square wave generator. It can be done by replacing the constant resistor and capacitor with variable resistor and variable capacitor.

5) Duty Cycle = $(PW/T) \times 100\%$. So, we can change the duty cycle of a circuit by ^{changing} ~~increasing~~ the pulse width or time period.

