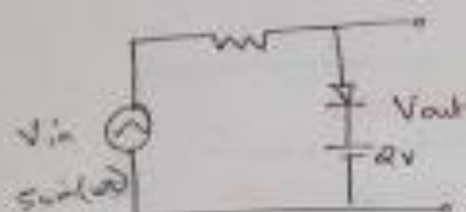





Clippers → cutting the signal between a particular range.

Clamper → moving the signal up or down.

POSITIVE CLIPPER





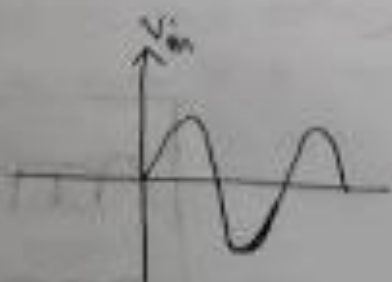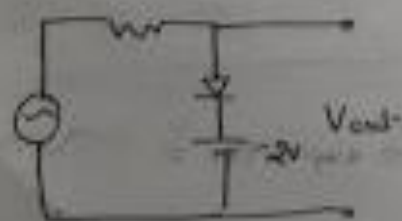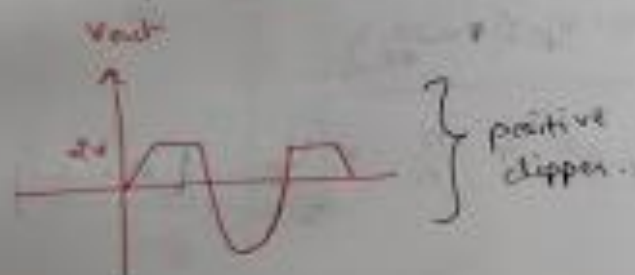- at 1V in V_{in} , diode is open so V_{out} will be whatever is V_{in} .
- same at 1.5V, so $V_{out} = V_{in}$.
- at 2V, diode is on → for ideal diode, it is short circuit so V_{out} is 2V.
- for ideal, if $V_{in} > 2V$ then $V_{out} = 2V$.




using 2V clipper.
as long as $V_{in} < -2$,
open circuit so $V_{in} = V_{out}$.
as long as $V_{in} > -2$, short-
circuit so $V_{out} = -2V$.

NEGATIVE CLIPPER

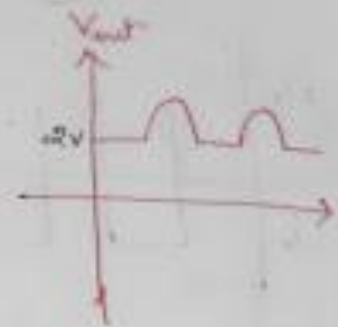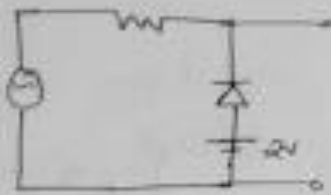

$V_{in} < 2V$, short circuit so $2V$.






$V_{in} > 2V$, open circuit so $V_{in} = V_{out}$.



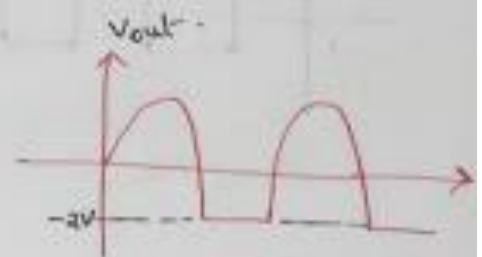

$$V_{in} < -2V, V_{out} = -2V$$
$$V_{in} > -2V, \quad V_{out} \rightarrow V_{in}$$

- ④ limit 'er upore pass korte para \rightarrow negative clipper




- ④ $u \quad u \quad \text{niebe} \quad u \quad u \quad u \rightarrow \text{positive clipper}$

input

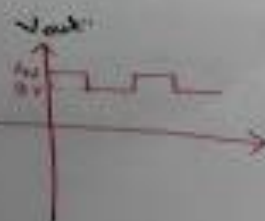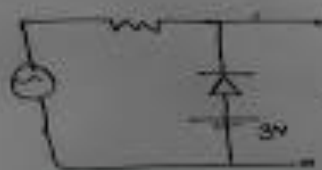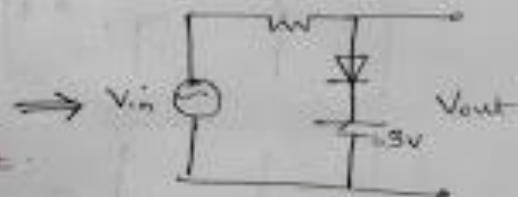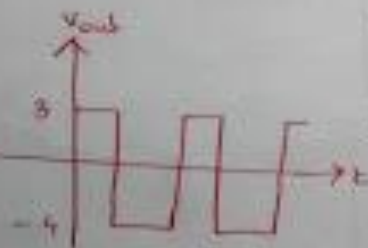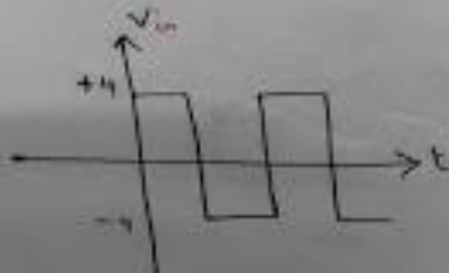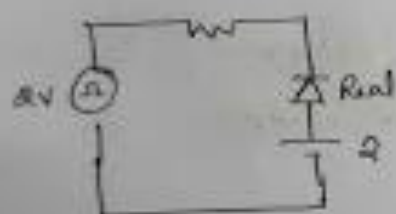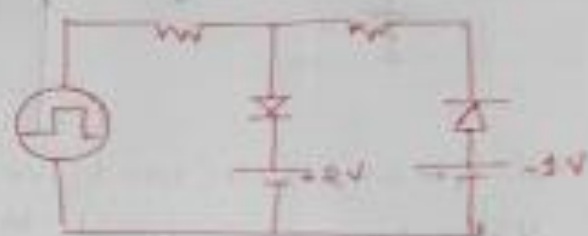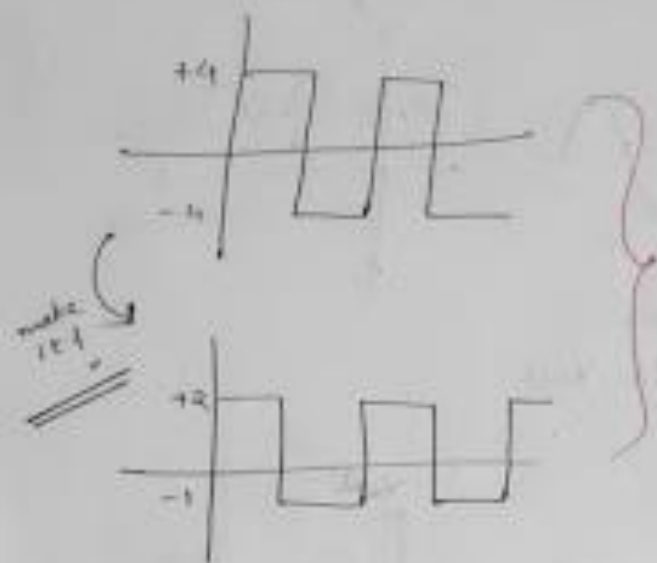



\Rightarrow

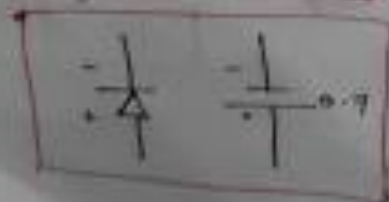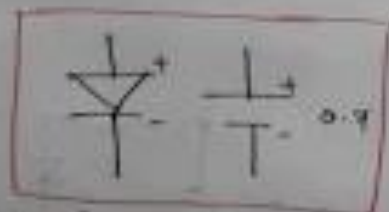
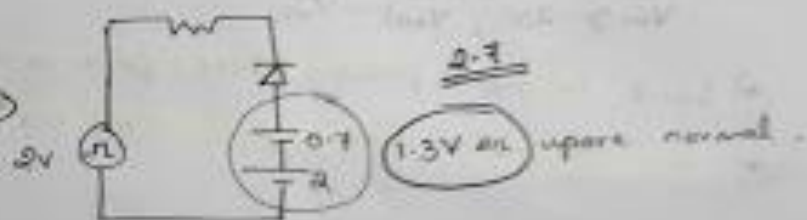


CLAMPER




at 3V, diode is ON, capacitor stores charge of 1V.

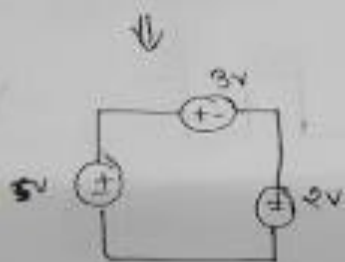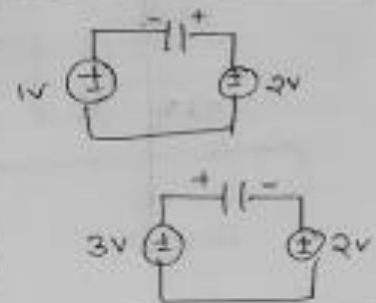current cannot flow, so capacitor will stay charged and the diode stays off.




negative clamping

upper peak becomes voltage given

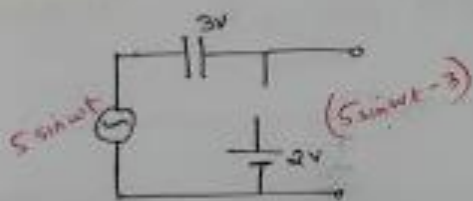

peak comes down to whatever is the value of voltage source.


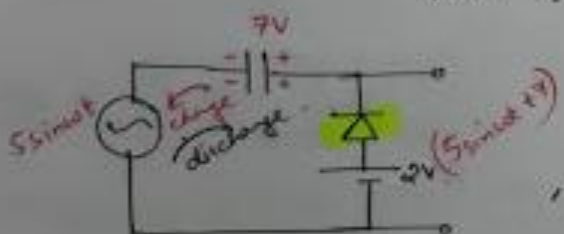
open circuit because right is 3+2=5V so Vin < 5V
hence open circuit since diode does not allow current flow.






stays constant at 7V → the capacitor.


positive clamping

lower peak becomes given voltage

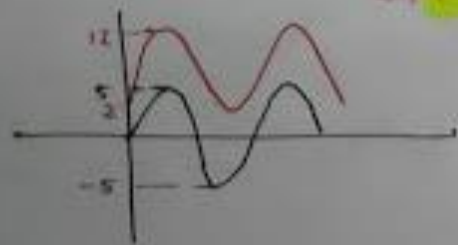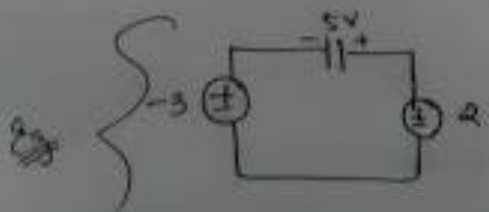


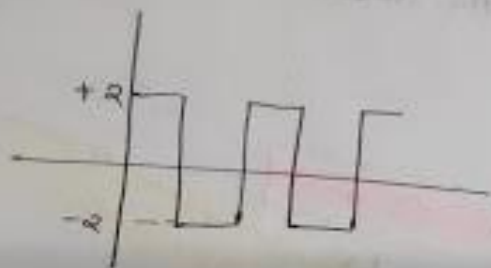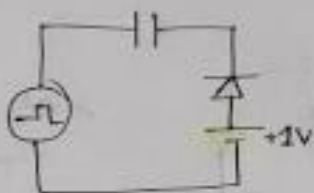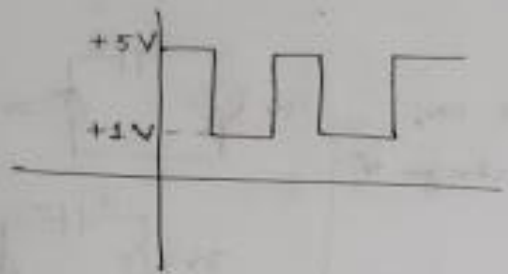

make it

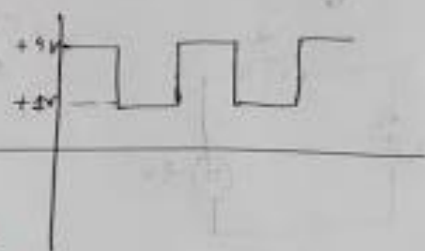

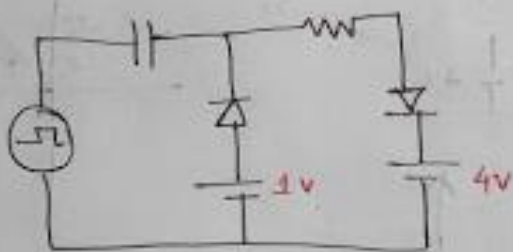first we
clamped
to +1 from
-2, then top
peak goes to
+5 so clip
it to +4V



first clip &
then clamp

