



Power dissipation of RTL circuit

Case 1: When input is 0V.

$$i_C = i_B = i_E = 0$$

$$i_B = 0$$
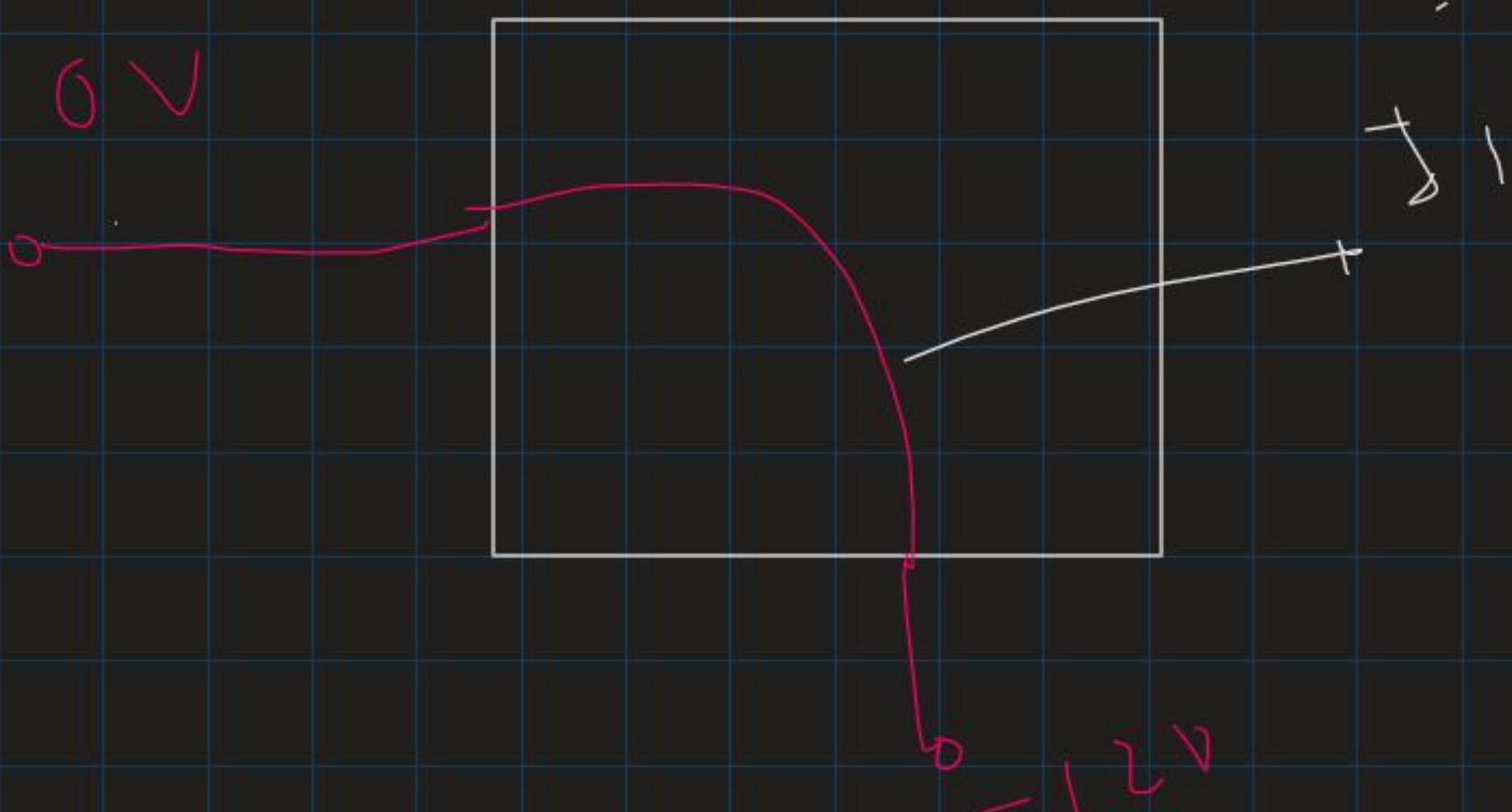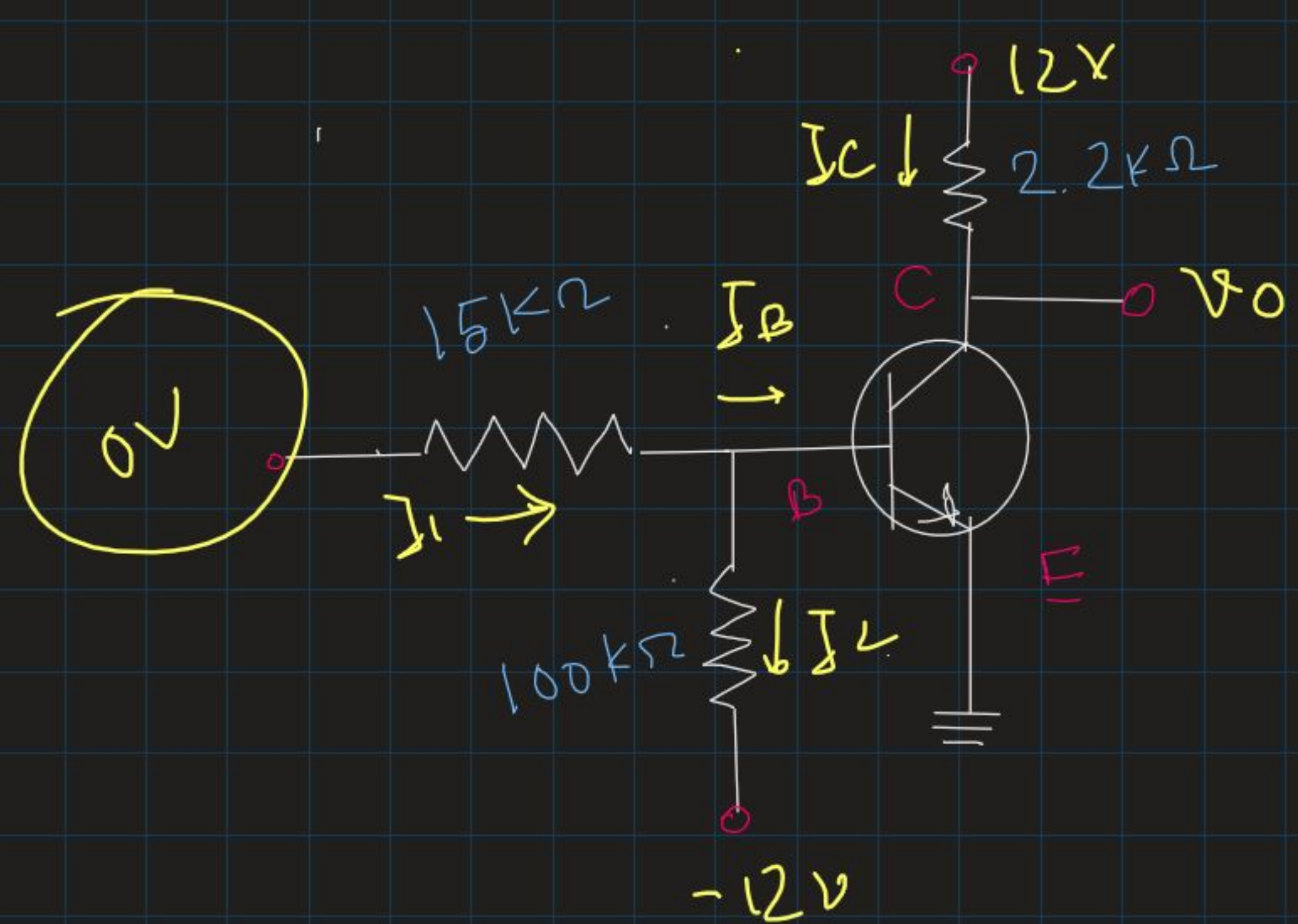
$$I_1 = I_2 = \frac{0 - (-12)}{100 + 15K} = 0.104 \text{ mA}$$



$$P = \Delta V \times I$$

$$= \{0 - (-12)\} \times 0.104 \text{ mW}$$

$$= 1.2521 \text{ mW}$$

Case 2: When input is 12Volt.

$Q \rightarrow$  saturation

$$V_B = 0.8 \text{ Volt}$$


$$V_C = 0.2 \text{ Volt}$$

$$V_E = 0$$

$$I_C = \frac{12 - 0.2}{2.2K} = 5.3636 \text{ mA}$$

$$I_1 = \frac{12 - 0.8}{15K} = 0.7466 \text{ mA}$$

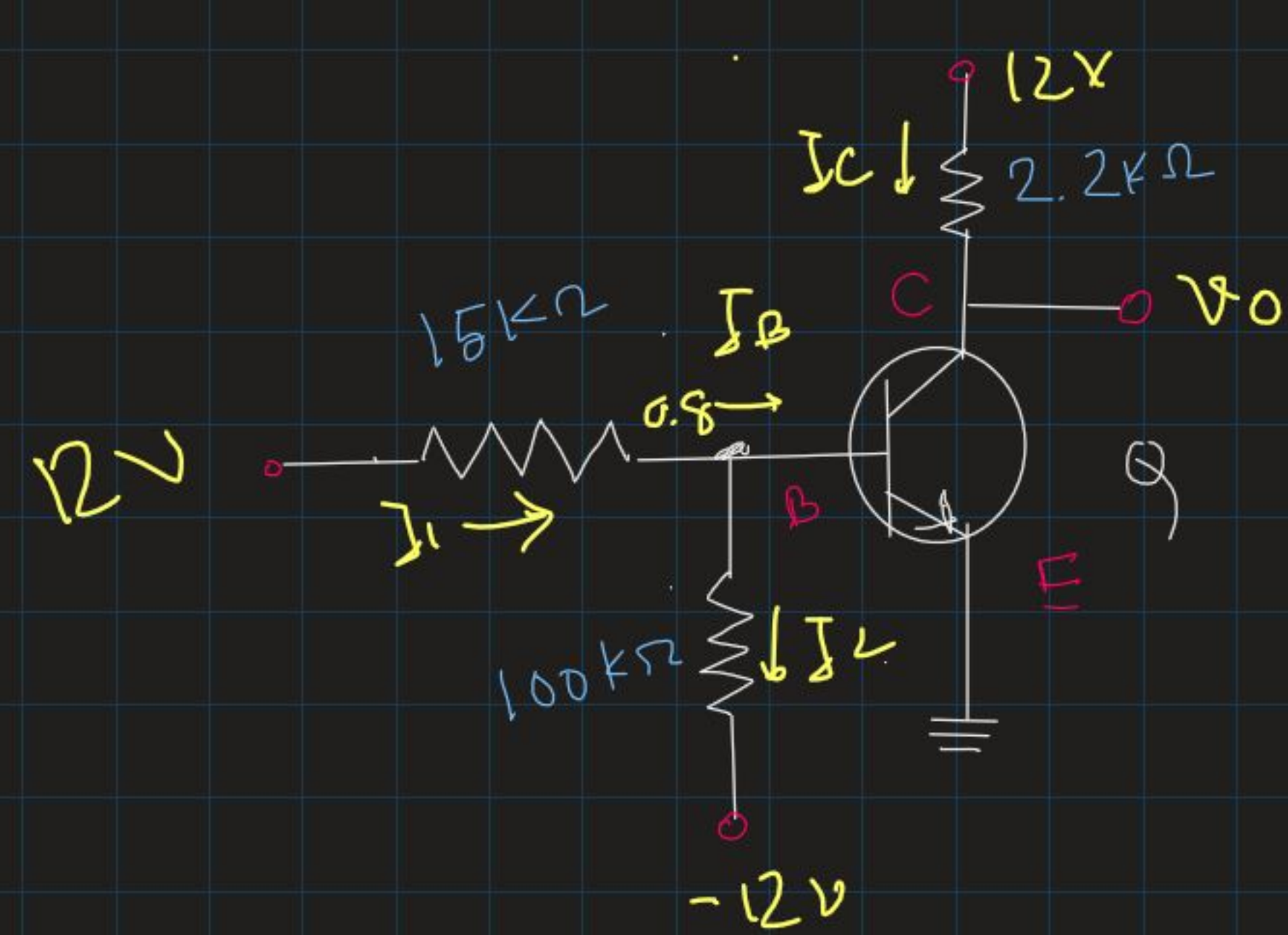
$$I_2 = \frac{0.8 - (-12)}{100K} = 0.128 \text{ mA}$$



using KCL

$$I_1 = I_2 + I_B$$
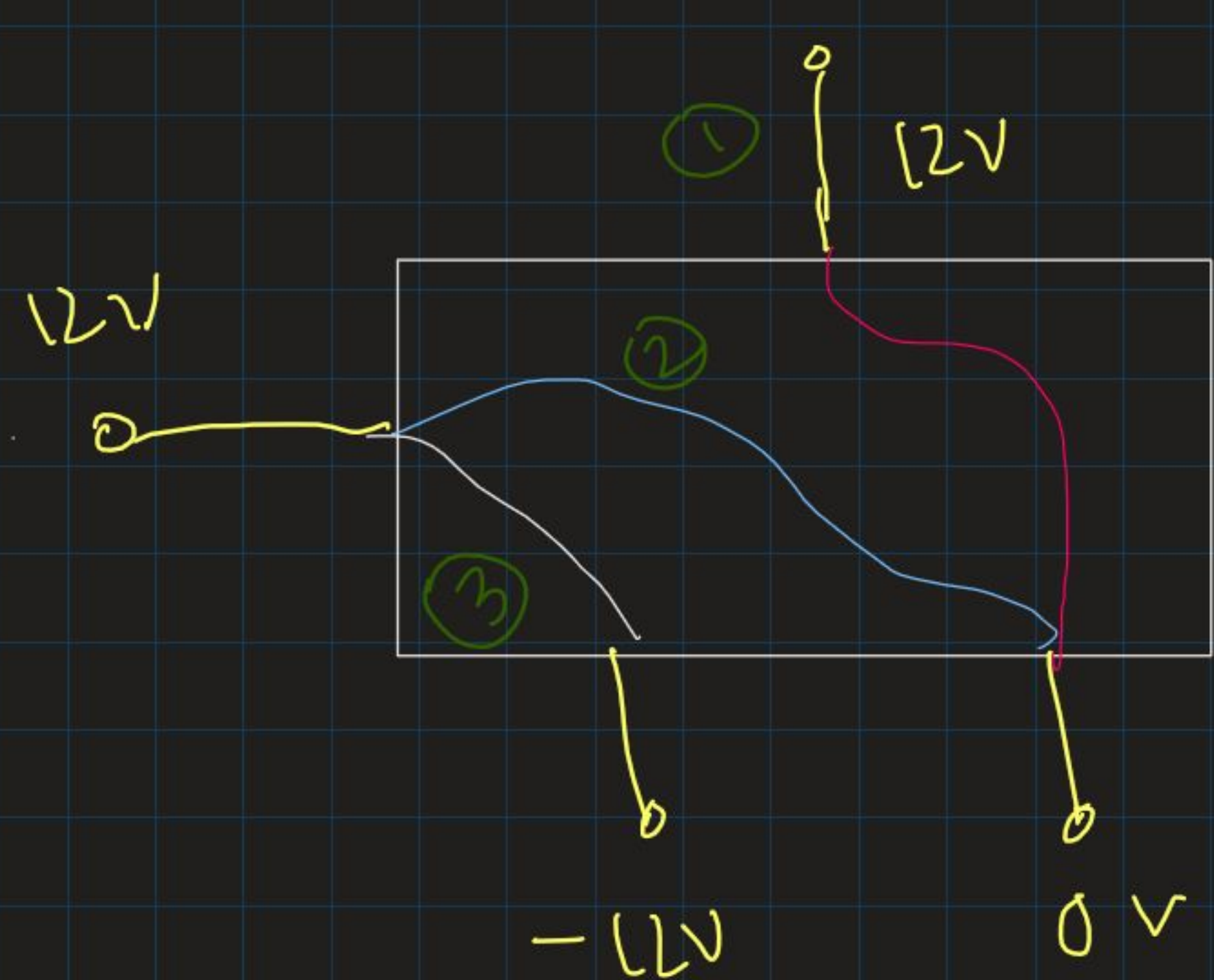
$$\Rightarrow I_B = I_1 - I_2 = 0.7466 \text{ mA} - 0.128 \text{ mA} = 0.6186 \text{ mA}$$



$$P_1 = \Delta V \times I_C$$

$$= (12 - 0) \times 5.3636 \text{ mW}$$

$$= 64.3632 \text{ mW}$$

$$P_2 = \Delta V \times I_B$$

$$= (12 - 0) \times 0.6186 \text{ mW}$$

$$= 7.4232 \text{ mW}$$

$$P_3 = \Delta V \times I_C$$

$$= \{12 - (-12)\} \times 0.128 \text{ mW}$$

$$= 3.072 \text{ mW}$$

$$P = P_1 + P_2 + P_3 = 74.8584 \text{ mW}$$

Average Power Dissipation

$$P = V_{CC} \times I_{CC}$$

$$P_{AV} = \frac{P_{C1} + P_{C2}}{2}$$



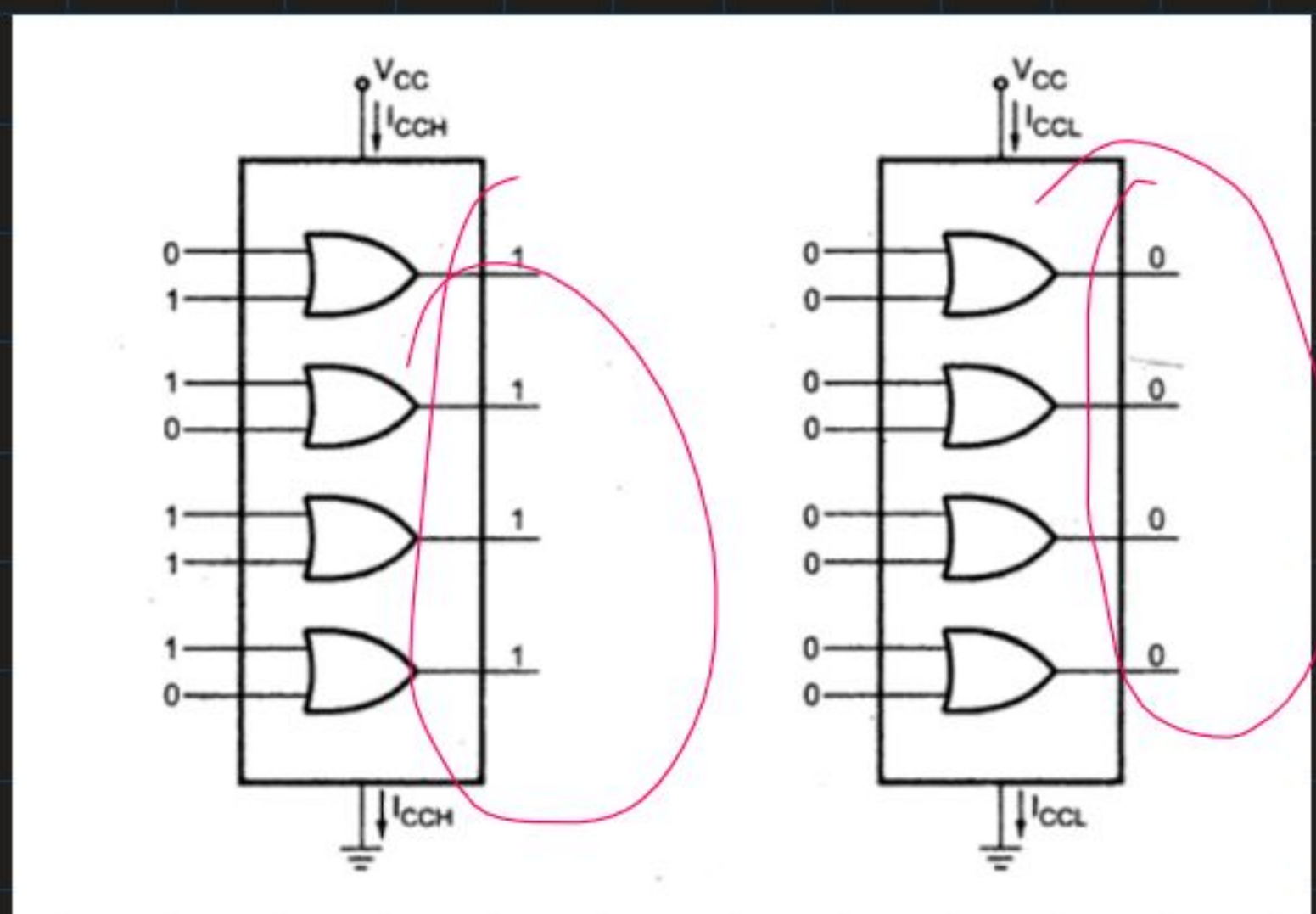


Figure of merit (PJ) = propagation delay  $\times$  power.

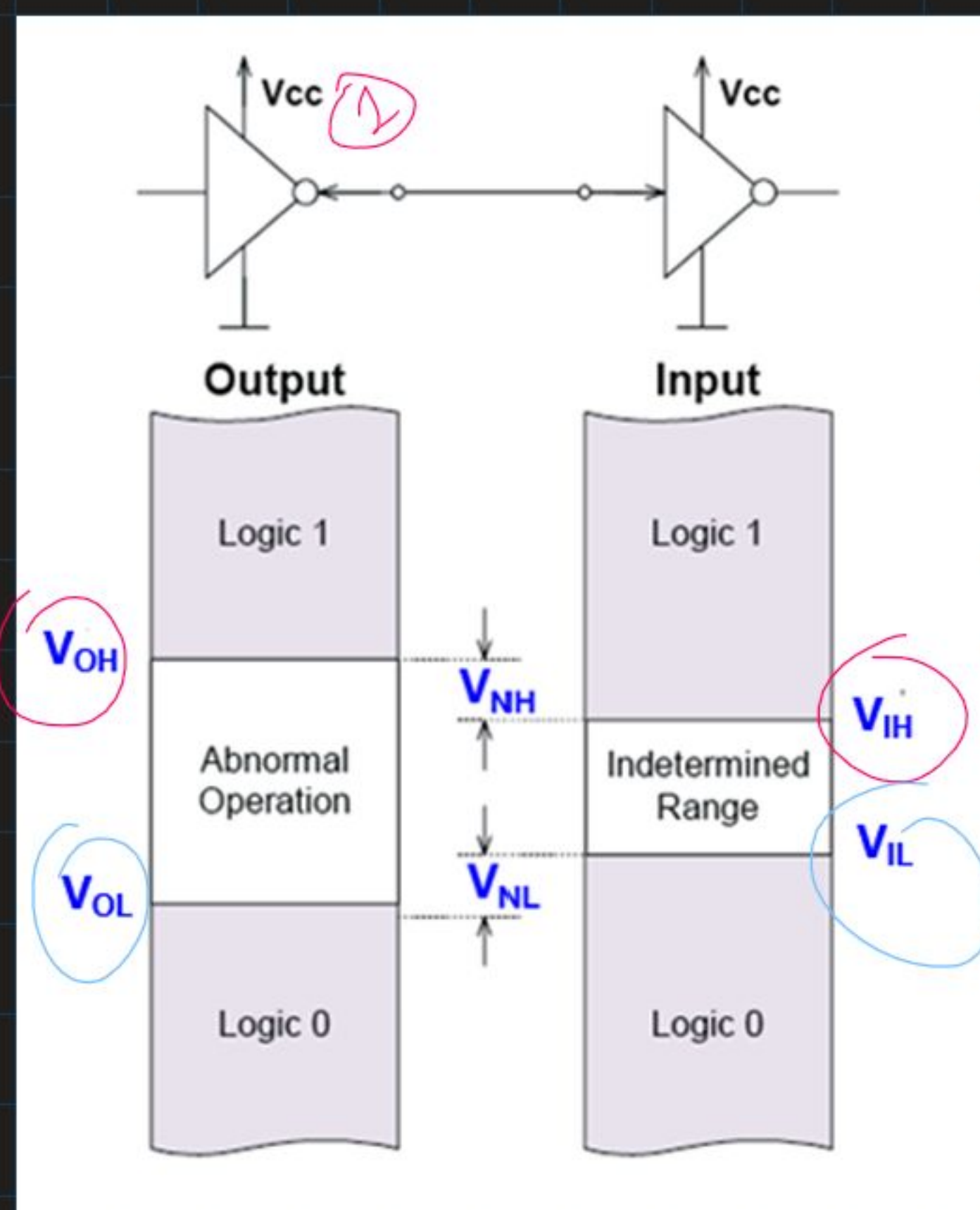

- $V_{OH}(\min)$  – The minimum voltage level at an output in the logical “1” state under defined load conditions
- $V_{OL}(\max)$  – The maximum voltage level at an output in the logical “0” state under defined load conditions
- $V_{IH}(\min)$  – The minimum voltage required at an input to be recognized as “1” logical state
- $V_{IL}(\max)$  – The maximum voltage required at an input that still will be recognized as “0” logical state

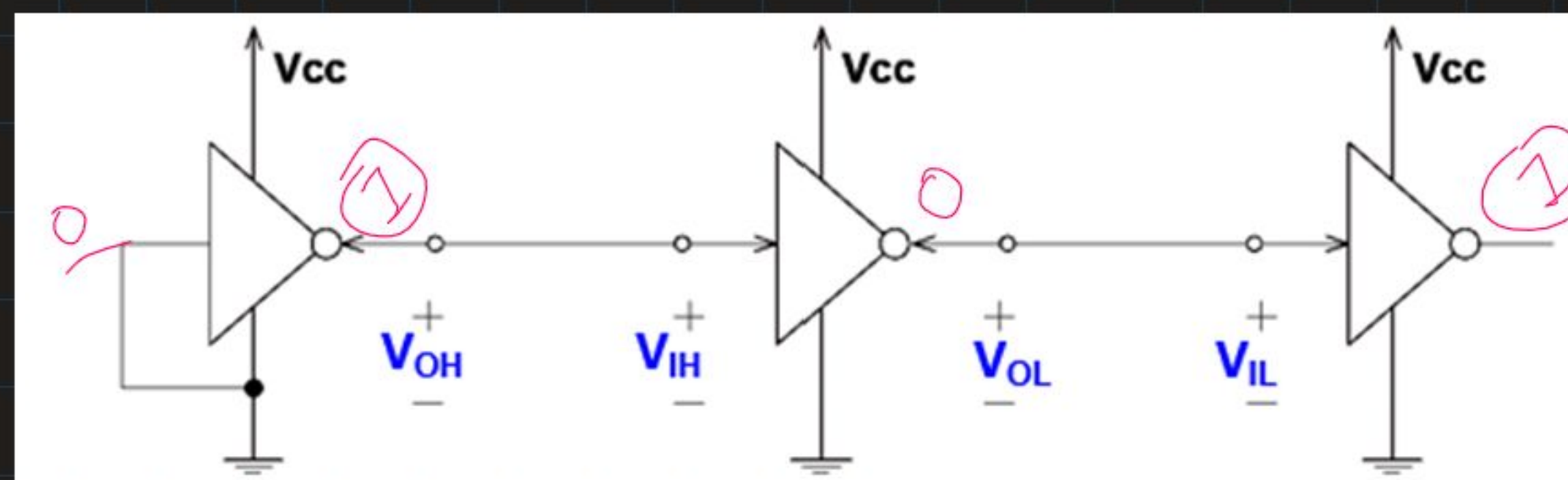

**HIGH state noise margin:**

$$V_{NH} = V_{OH}(\min) - V_{IH}(\min)$$

**LOW state noise margin:**

$$V_{NL} = V_{IL}(\max) - V_{OL}(\max)$$

**Noise margin:**

$$V_N = \min(V_{NH}, V_{NL})$$

$$\left\{ \begin{array}{l} V_{OH} > V_{IH} \\ V_{IL} > V_{OL} \end{array} \right.$$



$$V_{OL} = 0.2V$$

$$V_{OH} = (12 - 0.5)V$$

$$= 11.5V$$

V<sub>JL</sub> calculation


$$I_B = 0$$

$$I_2 = \frac{0.5 - (-12)V}{100K} = 0.125mA$$

$$I_1 = I_2$$

$$I_1 = \frac{V - 0.5}{15K} = 0.125mA$$

$$V = 2.375V \text{ or } V_{JL}$$

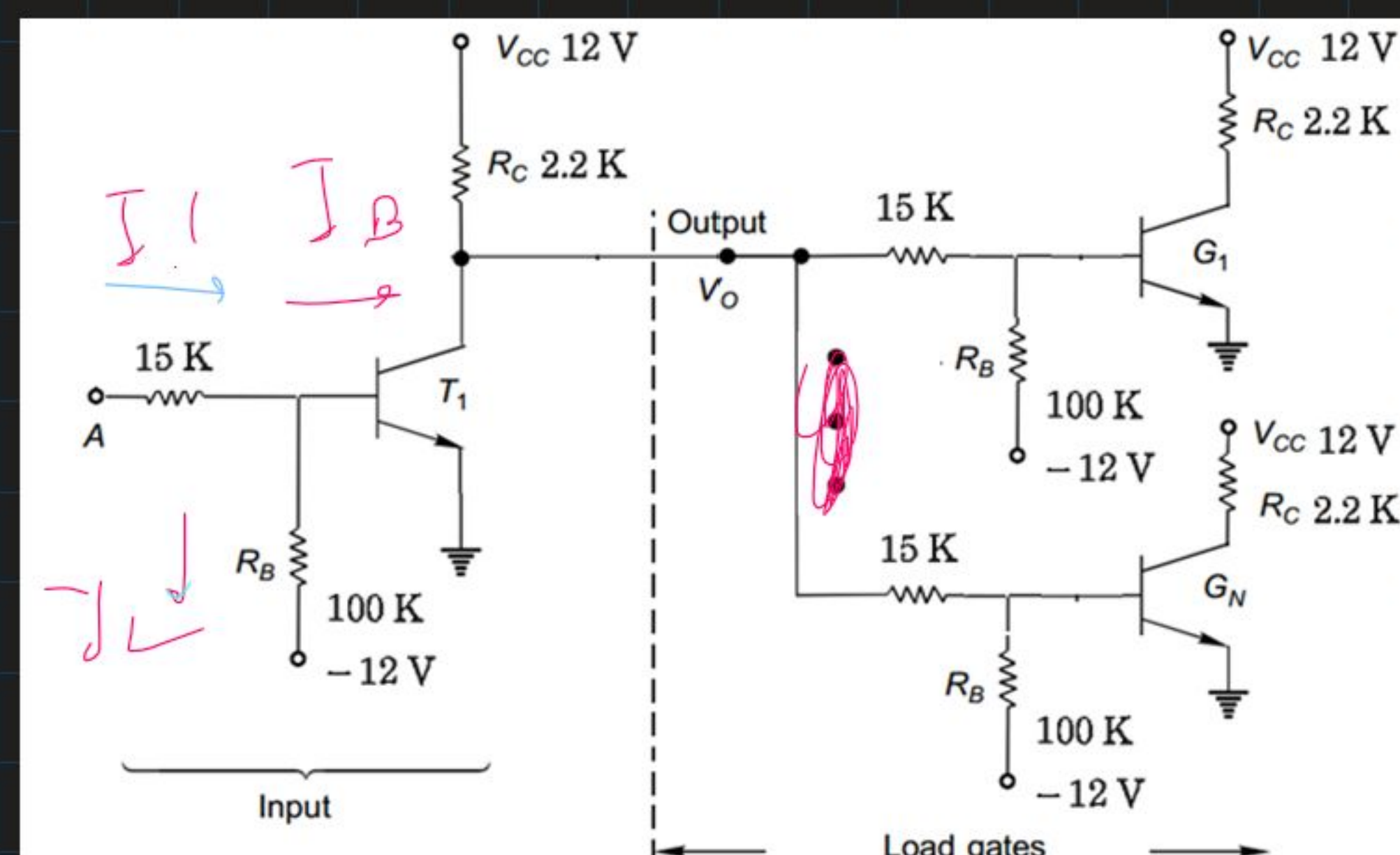

$$V_{TH} = ?$$

T1 → saturation

saturation → active

V<sub>TH</sub> → transition point

$$V_B = 0.8V$$

$$I_C = \beta_F \times I_B$$

$$V_C = 0.2V$$

$$I_C = \frac{12 - 0.2}{2.2K} = 5.3636mA$$


$$I_B = \frac{I_C}{\beta_F} = \frac{5.3636}{30} mA = 0.1788mA$$

$$I_2 = \frac{0.8 - (-12)}{100K} = 0.128mA$$

$$I_1 = I_2 + I_B = (0.128 + 0.1788) mA = 0.3068mA$$

$$I_1 = \frac{V - 0.8}{15K} = 0.3068mA$$

$$V = 5.4018V = V_{JH}$$

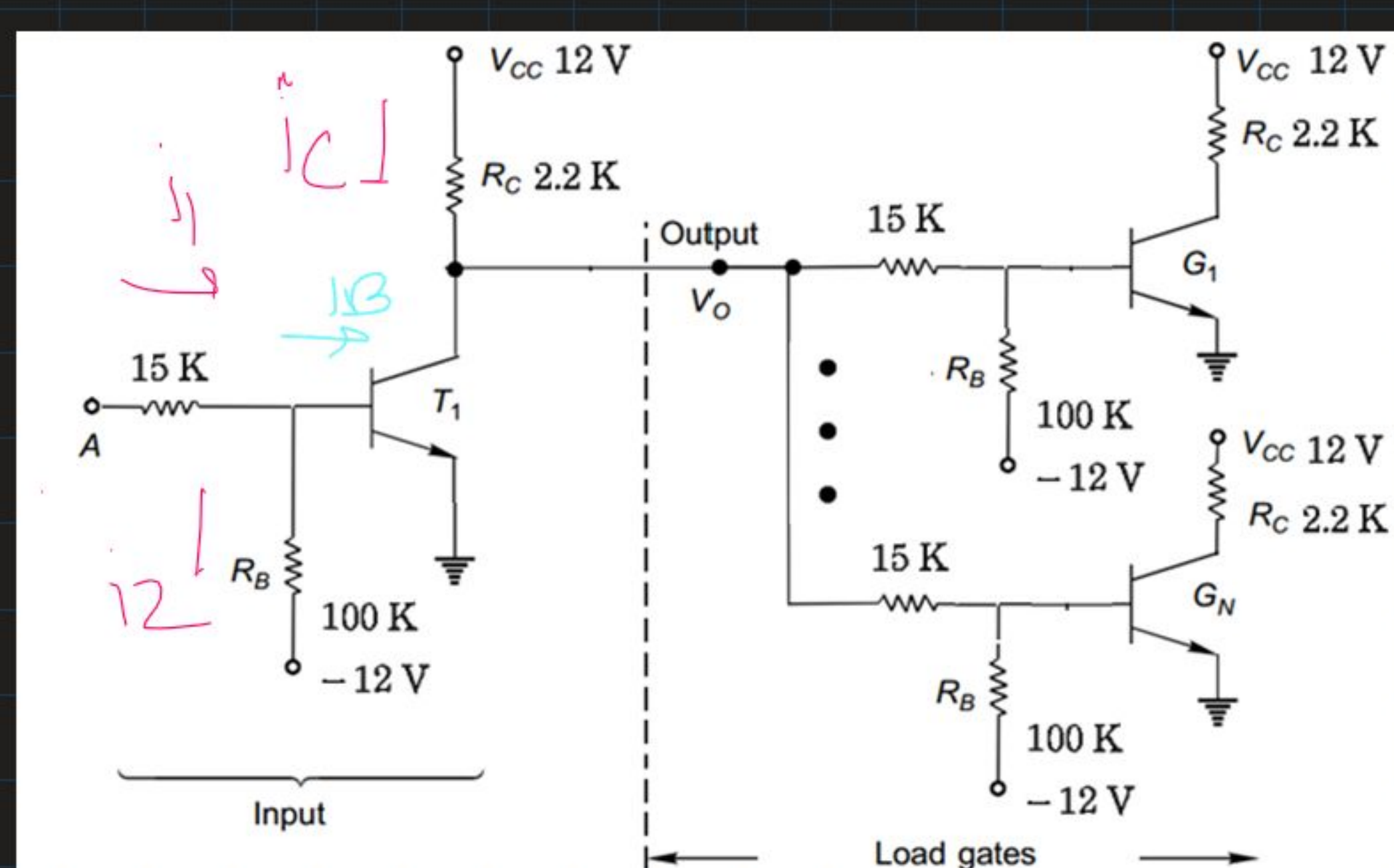

HIGH state noise margin:  
 $V_{NH} = V_{OH}(\min) - V_{IH}(\min)$

LOW state noise margin:  
 $V_{NL} = V_{IL}(\max) - V_{OL}(\max)$

Noise margin:  
 $V_N = \min(V_{NH}, V_{NL})$

$$V_N = 2.173V$$

$$V_{NH} = 11.5V - 5.4018V = 6.0982V$$

$$V_{NL} = 2.375V - 0.2V = 2.173V$$



**Fanout:** the maximum number of logic inputs (of the same logic family) that an output can drive reliably

- $I_{IH}$  – Current flowing into an input when driver's output is at logical high
- $I_{IL}$  – Current flowing into an input when driver's output is at logical low
- $I_{OH}$  – Current flowing into an output in the logical “1” state under specified load conditions
- $I_{OL}$  – Current flowing into an output in the logical “0” state under specified load conditions

Calculate the fanout of this RTL circuit. Assume  $V_{OH} = 10$  Volt

1st case: When output is at 0.2 volt

Supply  $\rightarrow$  driver


Demand  $\rightarrow$  load

$$\text{Maximum total supply} = \frac{12 - 0.2}{2.2k} = 5.3636 \text{ mA}$$

$$\text{individual load current} = \frac{0.2 - (-12)}{(100 + 15)k} = 0.106 \text{ mA}$$

$$\text{Fanout} = \frac{5.3636}{0.106} = \lfloor 50.6 \rfloor = 50$$


When driver is at logical low

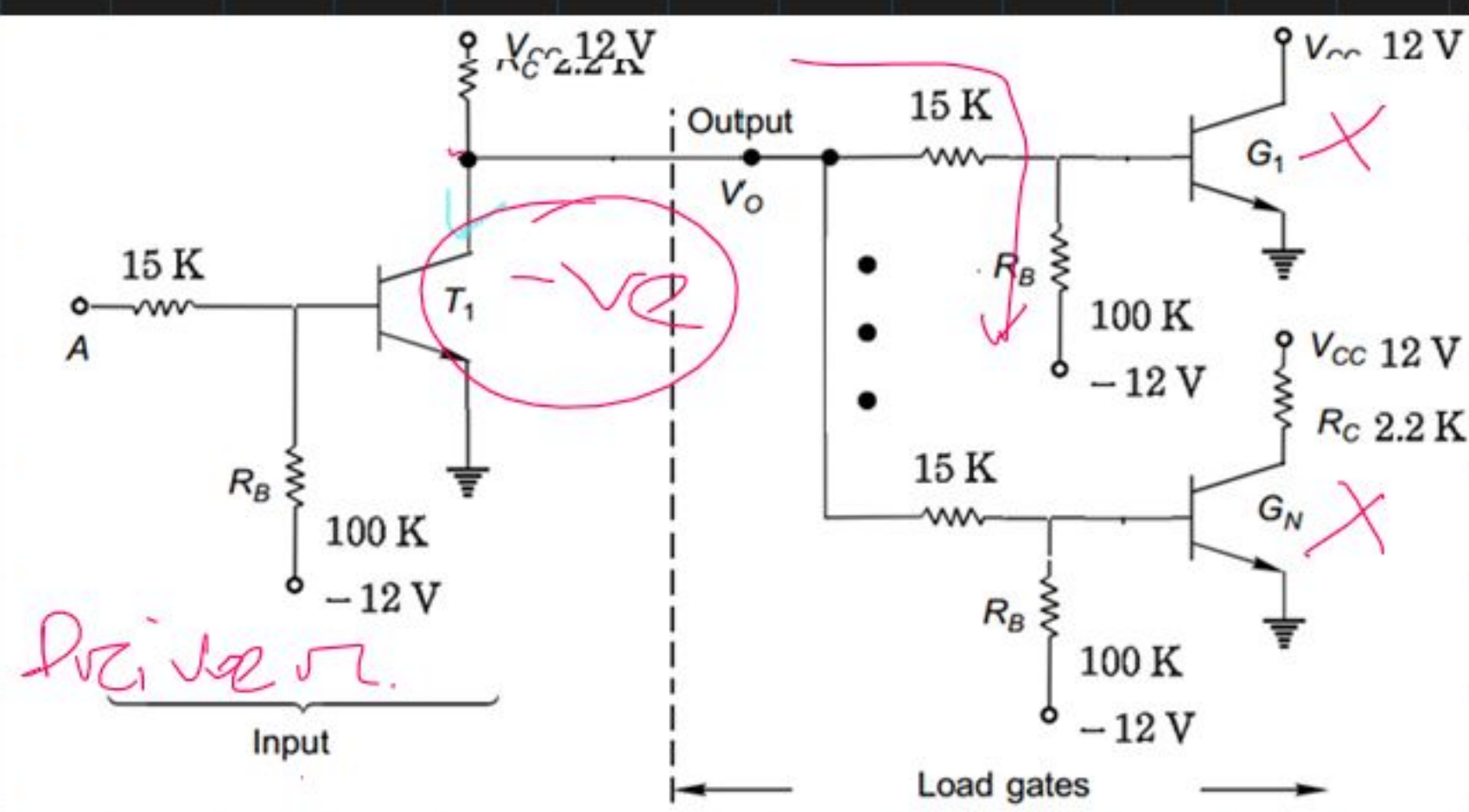

2nd case

$$V_{OH} = 10V$$
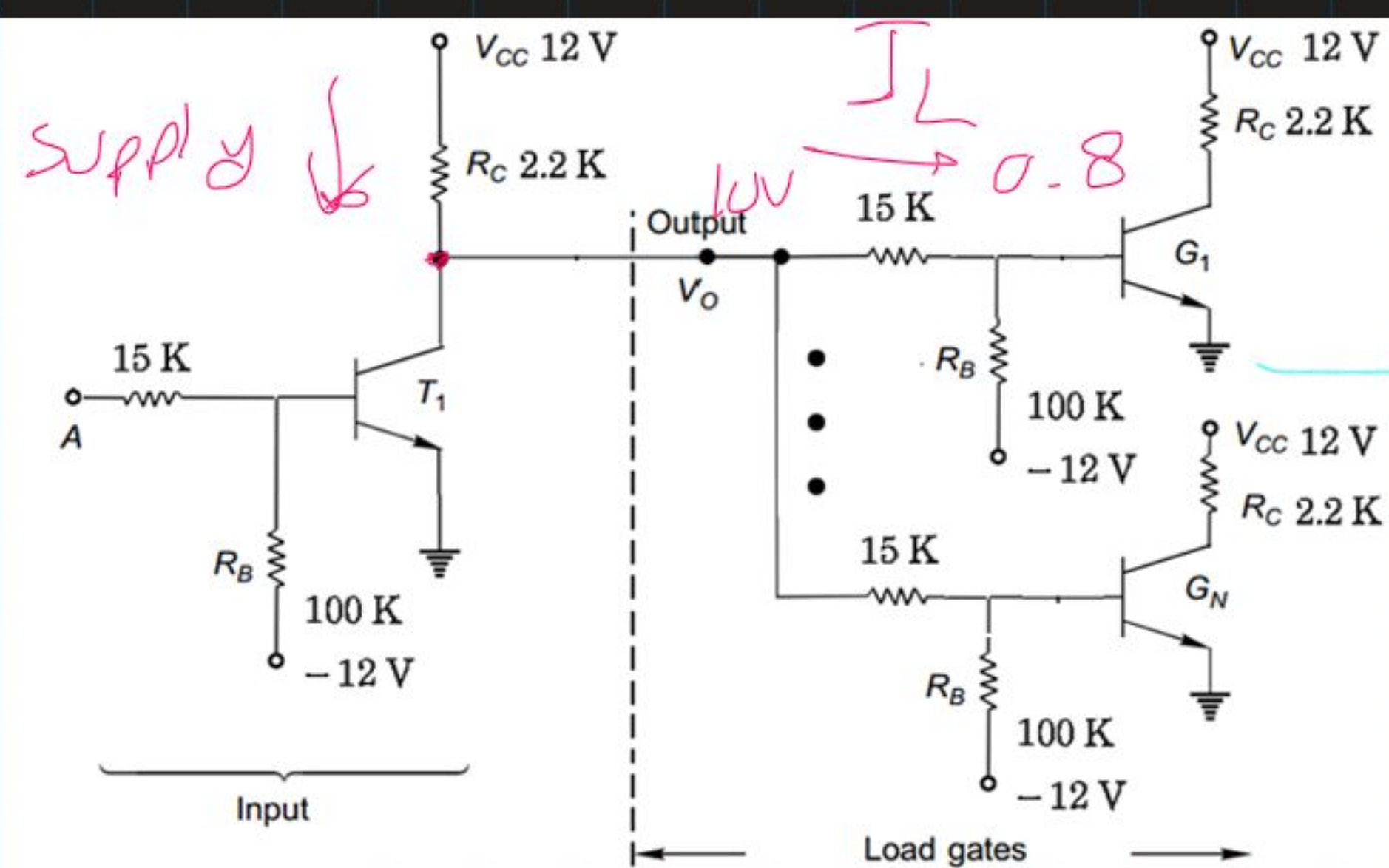
$$\text{Maximum total supply} = \frac{12 - 10}{2.2k} = 0.909 \text{ mA}$$



$$F = 0$$

\* load transistor will be in saturation

$$V_{BE} (\text{sat}) = 0.8V$$

$$* V_B = 0.8V$$

$$* \text{individual demand} = \frac{10 - 0.8}{15k} = 0.6133 \text{ mA}$$

$$\text{fanout} = \left\lfloor \frac{0.909}{0.6133} \right\rfloor = \lfloor 1.48 \rfloor = 1$$



$$\text{fanout} = 1$$

Worst case scenario during fanout calculation

$$\text{So, } \boxed{\text{fanout} = 1}$$



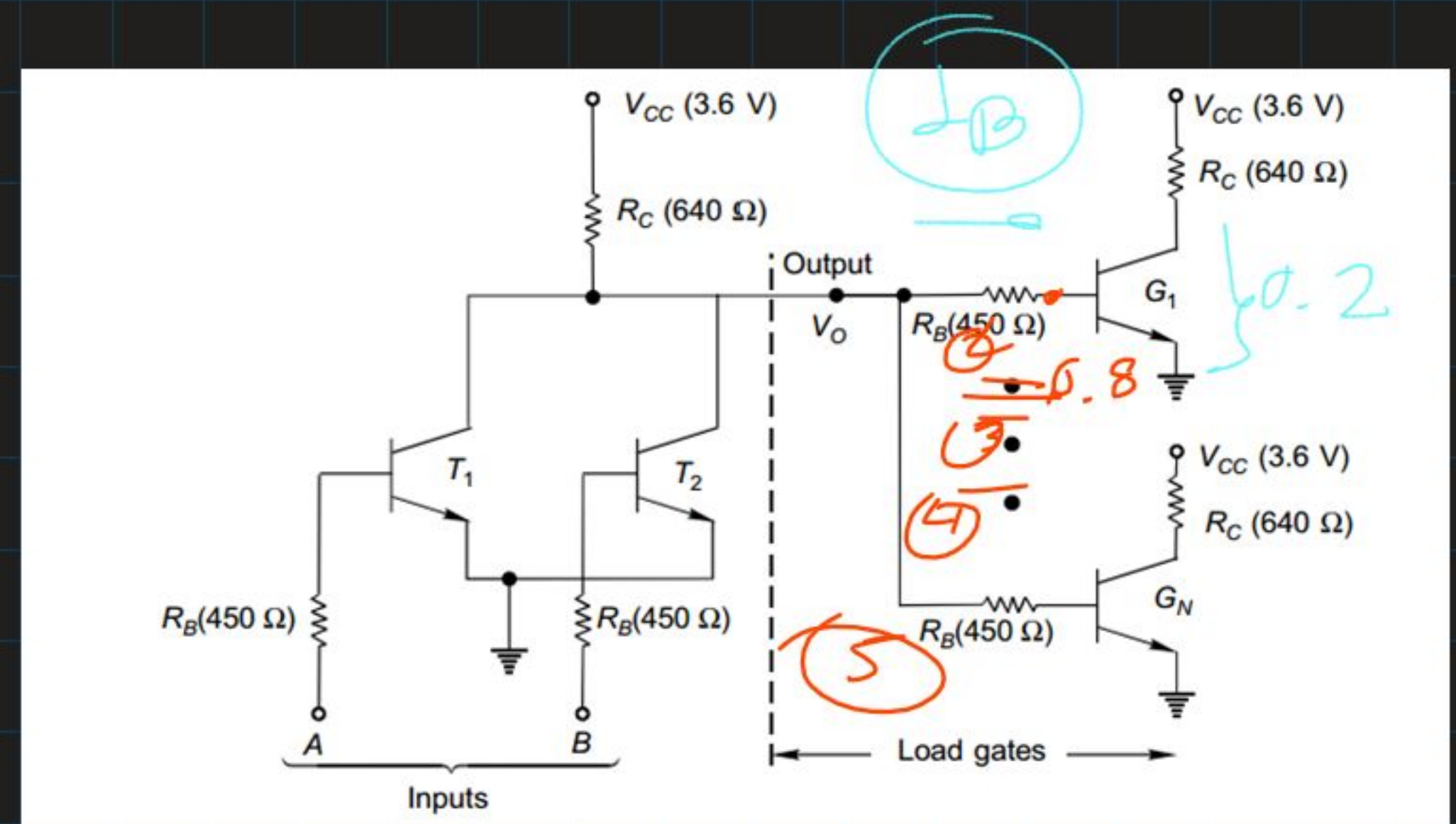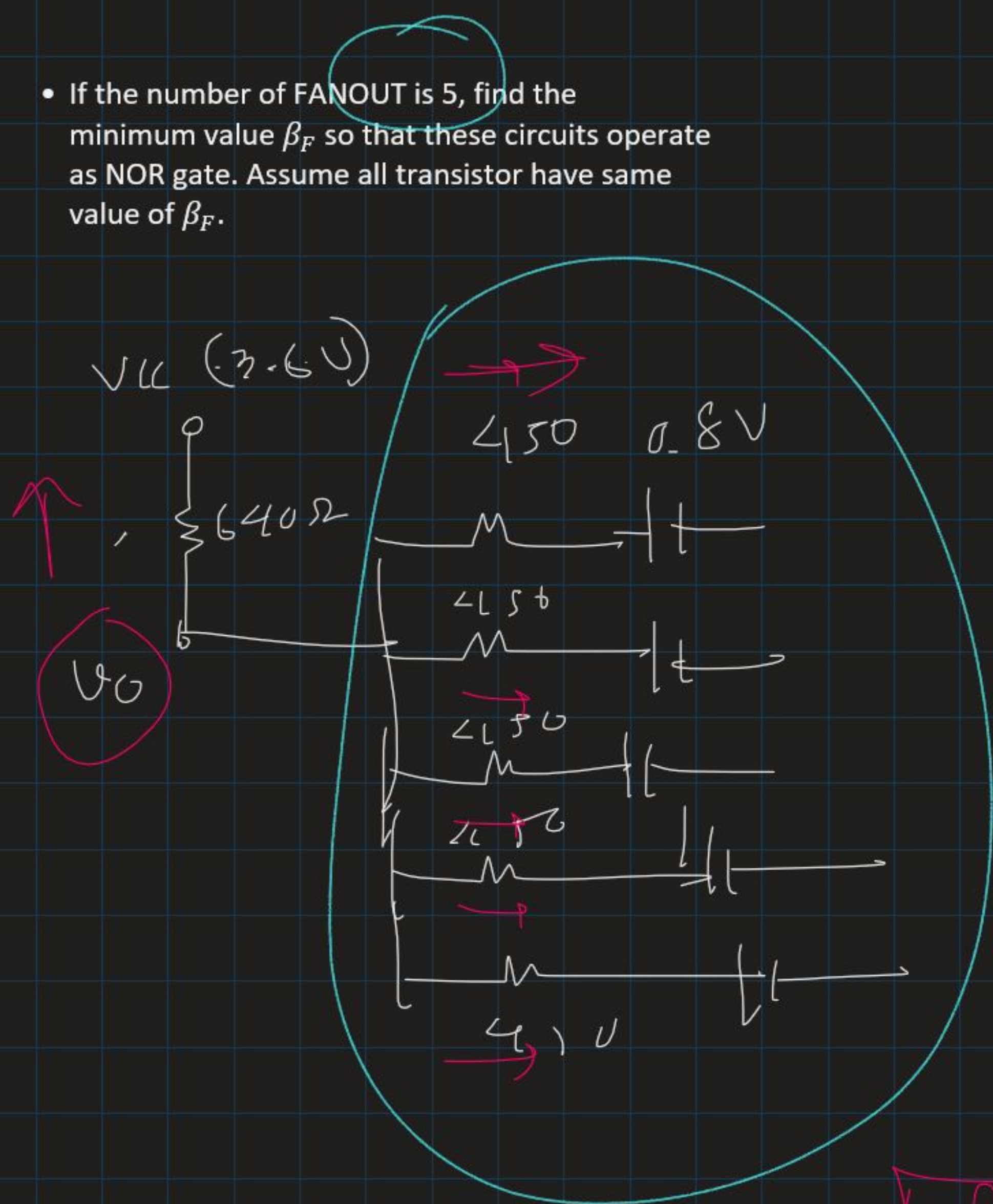- If the number of FANOUT is 5, find the minimum value  $\beta_F$  so that these circuits operate as NOR gate. Assume all transistor have same value of  $\beta_F$ .



$$V_O - 3.6 + \frac{V_O - 0.8}{0.45k} \times 5 = 0$$

$$V_O = 1.1452V$$

Forced

$$I_B = \frac{1.1452 - 0.8}{0.45k} = 0.767mA$$

So,  $V_C = 0.2V$

and so  $I_C = \frac{3.6 - 0.2}{0.64k\Omega} = 5.3125mA$

$$\beta_{forced} = \frac{I_C}{I_B} = \frac{5.3125}{0.767} = 6.9263$$

$$\beta_F > 6.9263$$



- Find the value for maximum FANOUT if  $V_{OH} = 2V$   
Given,  $\beta_F = 30$ .

1st case:

When  $v_i = 3.6V$

$$\text{total demand} = 0 \text{ mA}$$

Supply current =  $0 \text{ mA}$




$$\text{So, } \tan \alpha = \frac{6}{0}$$

### Second Case:

When  $V_1 = 0.2 \text{ V}$

$T_L \rightarrow$  forward active mode.

$V_0 \rightarrow$  logical high

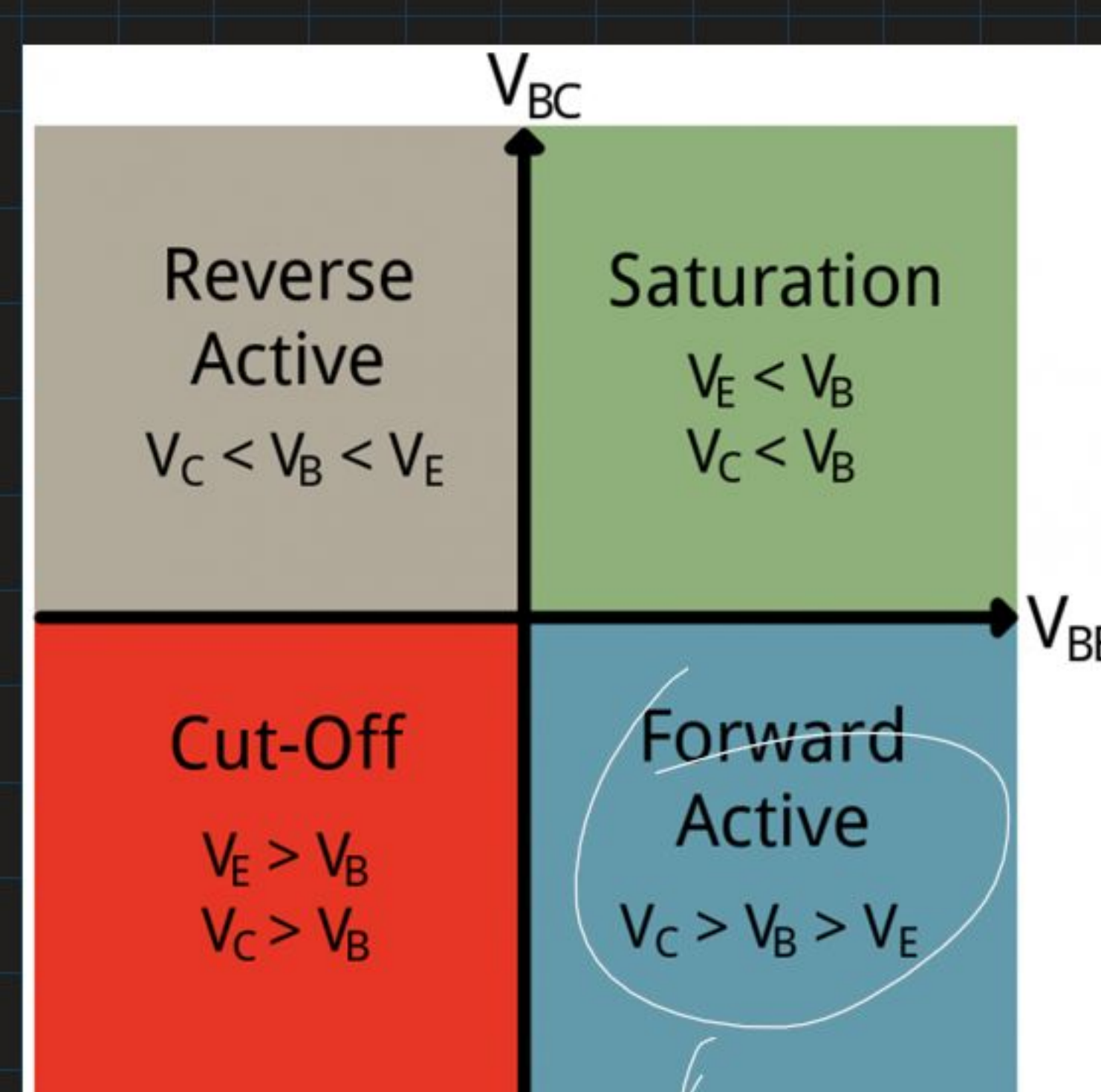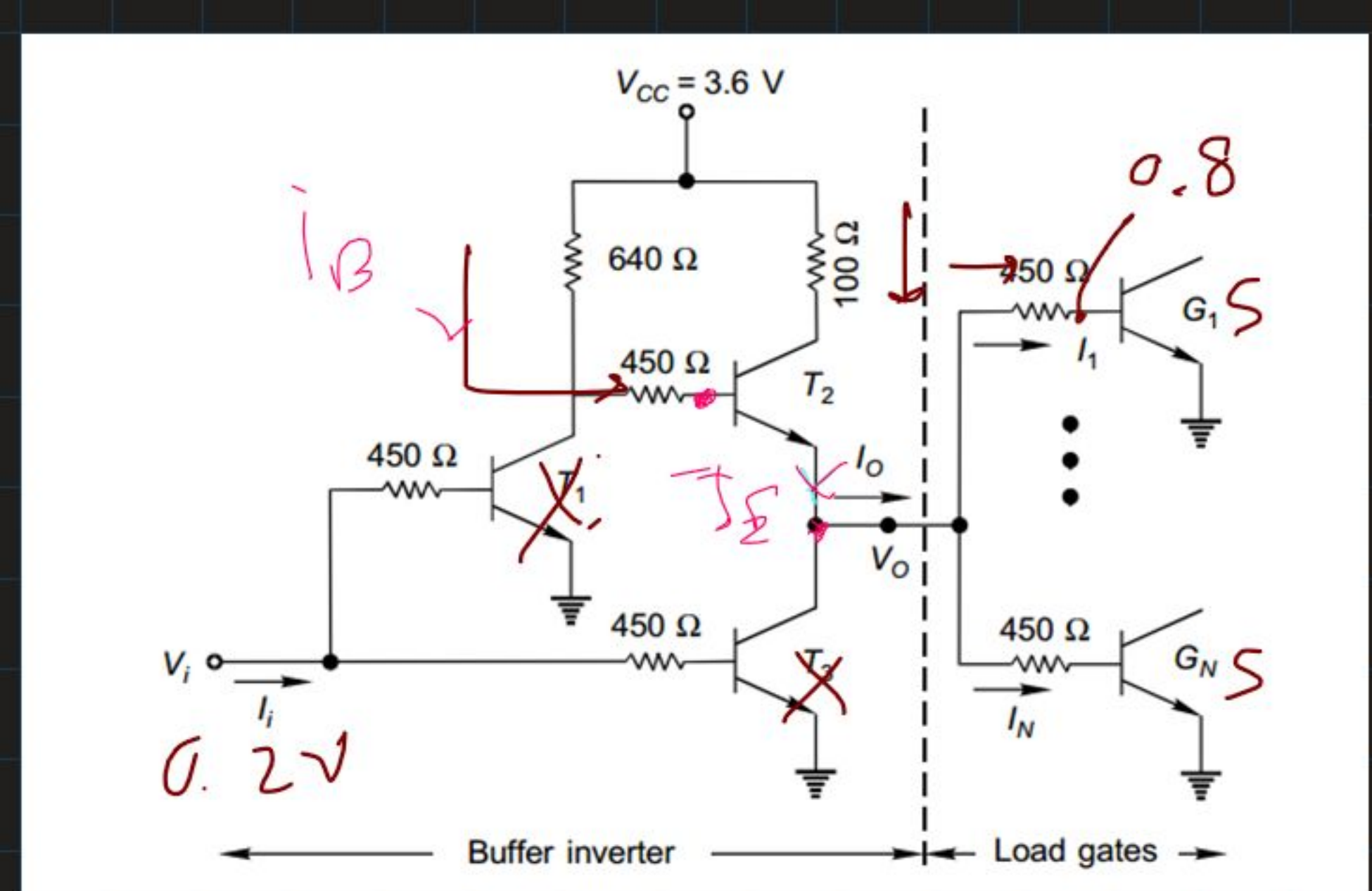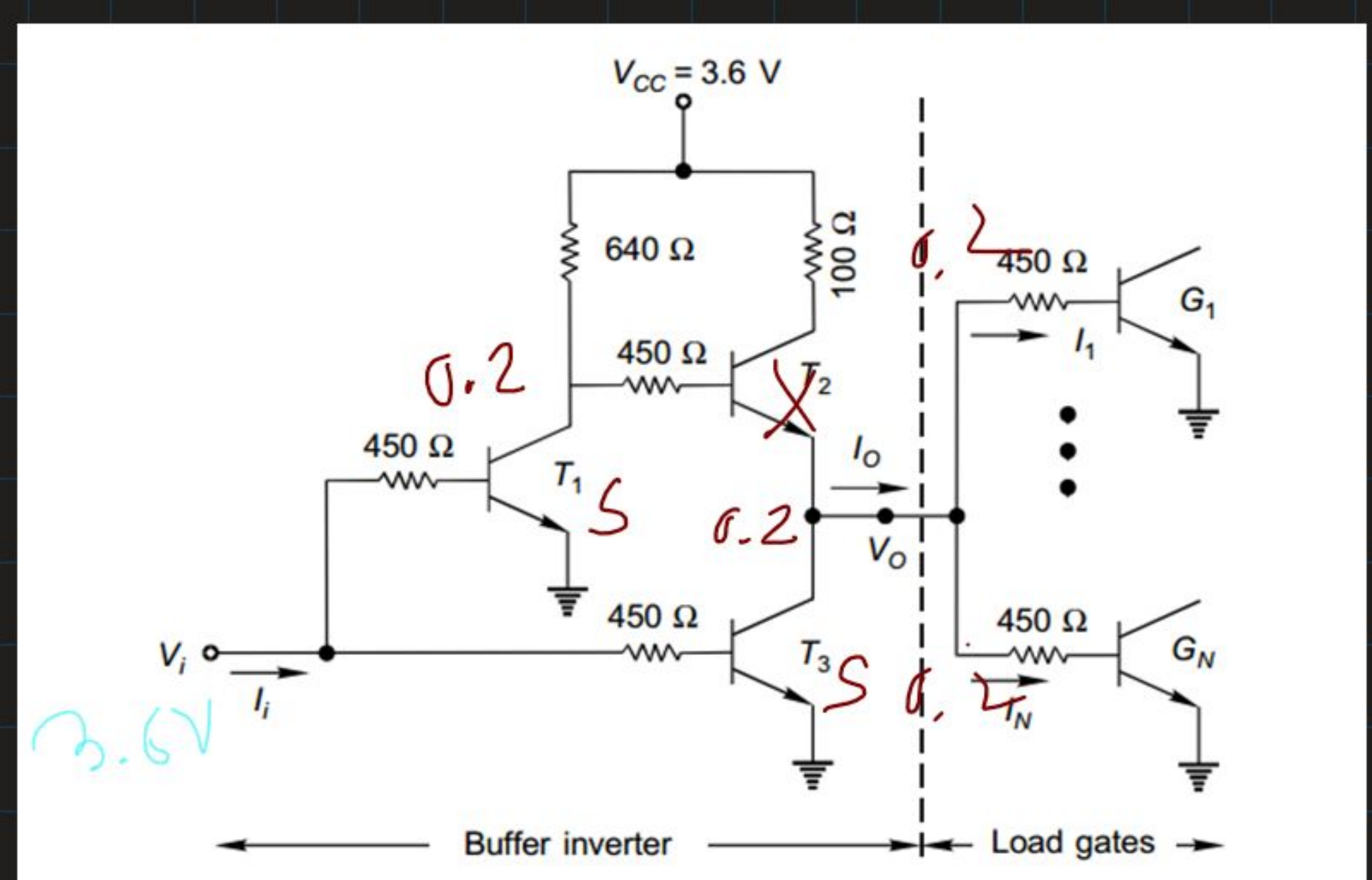

$$\sqrt{13} < \sqrt{14}$$

$$V_B < 0$$

$$\sqrt{B_F} \geq 0$$