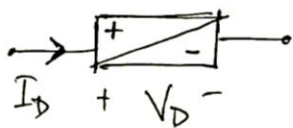



Transfer Characteristics

Till now, we have seen the I-V characteristics of devices.
This is the graph of the current of a device vs. its voltage.



Now, we will see another type of characteristics. If we plot any output parameter of a circuit (V_{out} , or, I_{out}) vs. any input parameter (V_{in} , or, I_{in}), the resulting graph is the transfer characteristics of that ckt.

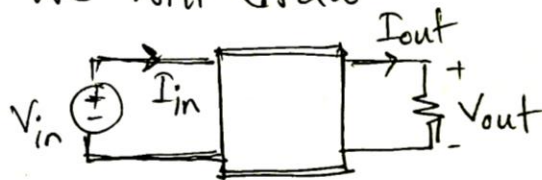[Note: We drew the I-V of a device, but, we will draw the Transfer Char. of a ckt]




The plot of V_{out} vs. V_{in} is called the Voltage Transfer characteristics (VTC) of a ckt.

The plot of I_{out} vs. I_{in} is called the Current Transfer characteristics (CTC) of a ckt.

The others (V_{out} vs. I_{in} , or, I_{out} vs. V_{in}) don't really have a special name. They are just called Transfer characteristics.

[4] We will ~~also~~ look at the VTC of some of the circuits we have studied until now.

(1) Voltage Divider:

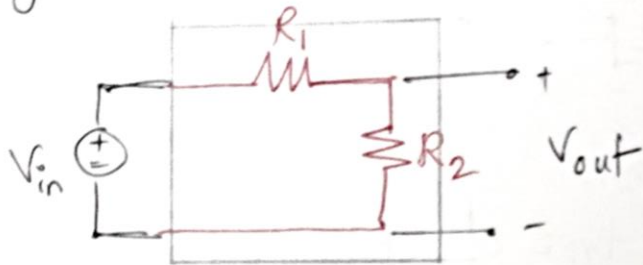


From Voltage-Division Rule, we have,

$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$


This is of the form $y = mx$ [If $y = V_{out}$, $x = V_{in}$]

\therefore The VTC looks like this:

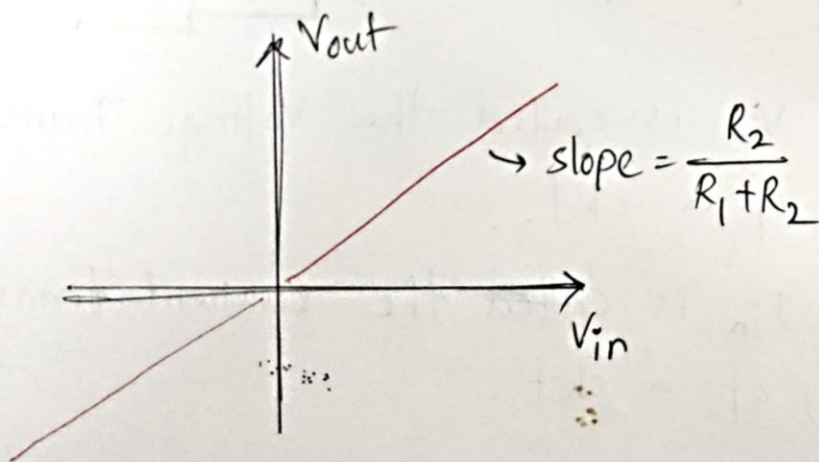


Note: For a Voltage Divider, slope of the VTC is less than 1. In fact, for any ckt with passive devices, the slope can be at most 1. For a slope higher than 1, (i.e., higher change in output than input, we will need an amplifier.

(2) Rectifier (Half-Wave):

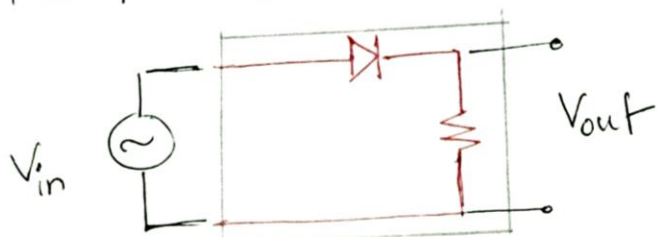

If the diode is ideal,
for +ve cycle, ($V_{in} > 0$), we have $V_{out} = V_{in}$ [\because diode is short]
for -ve cycle, ($V_{in} < 0$), we have $V_{out} = 0$ [\because diode is open].


The VTC will look like this:

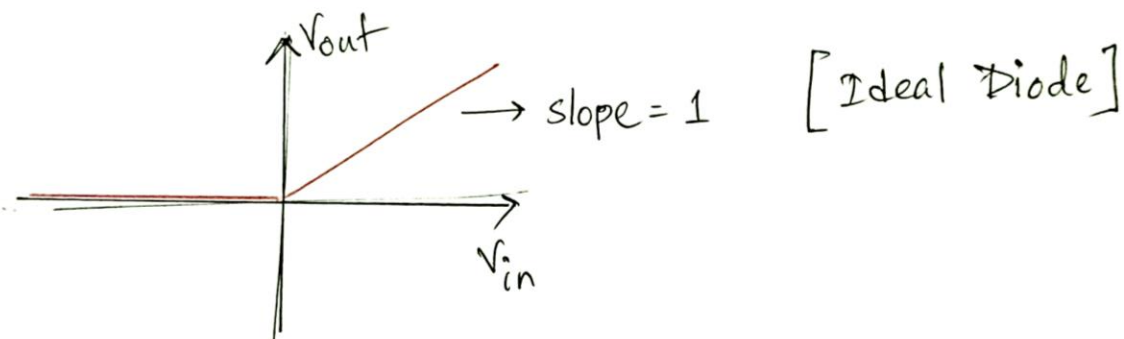


For real diodes, the diode will be ON, if the input ~~cross~~ surpasses $0.7V$. Also, the output will be $0.7V$ below the input.

$$\therefore \text{For } V_{in} > 0.7, \quad V_{out} = V_{in} - 0.7$$
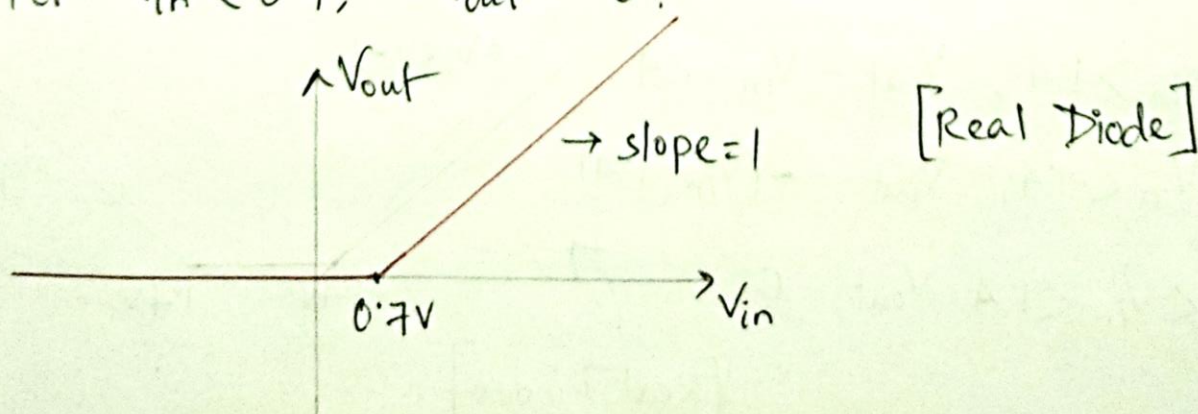
$$\text{for } V_{in} < 0.7, \quad V_{out} = 0.$$



(3) Rectifier (Full-Wave):

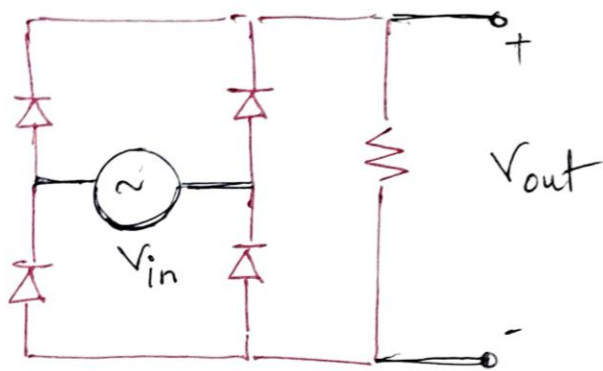


As before, for ~~the~~ ideal diodes,

For +ve cycle, ($V_{in} > 0$), $V_{out} = V_{in}$.

And for -ve cycle, ($V_{in} < 0$), the input will be flipped at the output. $\therefore V_{out} = -V_{in}$.

The VTC will be: \longrightarrow

[Ideal Diodes] \longrightarrow

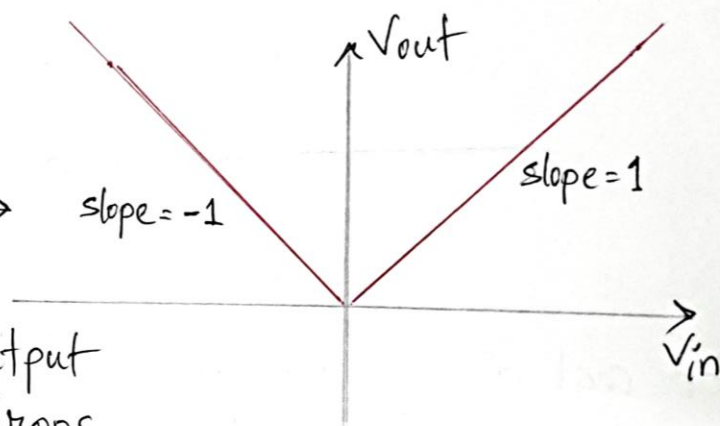

For real diodes, we will have output if the input surpasses 2 diode drops.

[\because 2 diodes will be active in any cycle].


And, the output will be 2 diode-drops below the input.

\therefore If $V_{in} > 1.4$, $V_{out} = V_{in} - 1.4$


If $V_{in} < -1.4$, $V_{out} = -(V_{in} - 1.4)$

For $-1.4 < V_{in} < 1.4$, $V_{out} = 0$.

[Real Diodes]

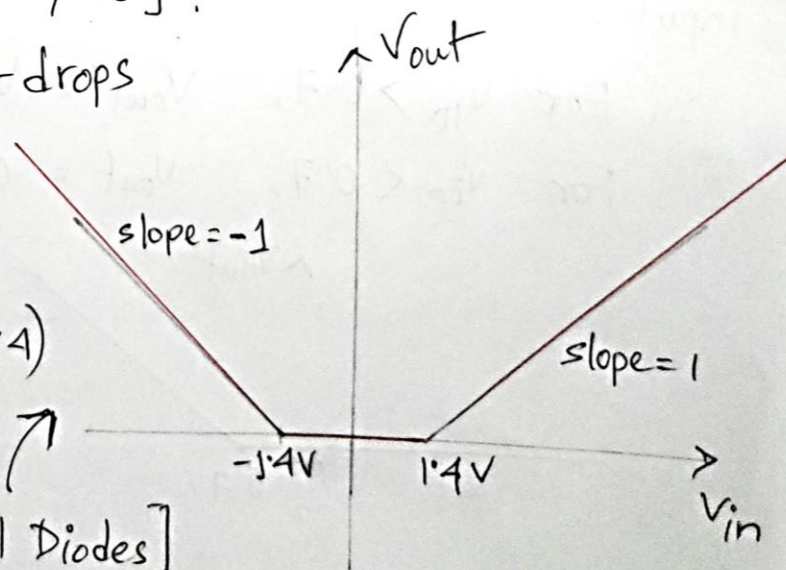


(4) Clipper Circuits:

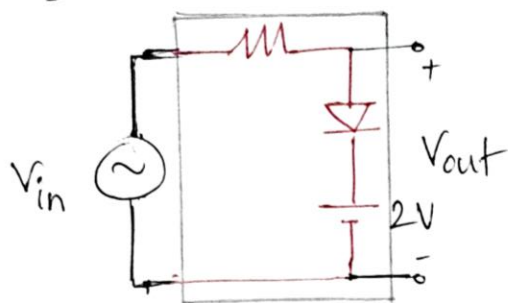



This ckt will pass everything below 2V as is. ~~For~~ All voltages above 2V will be clipped at 2V.

$$\therefore \text{If } V_{in} < 2V, V_{out} = V_{in}$$

$$\text{If } V_{in} > 2V, V_{out} = 2V$$

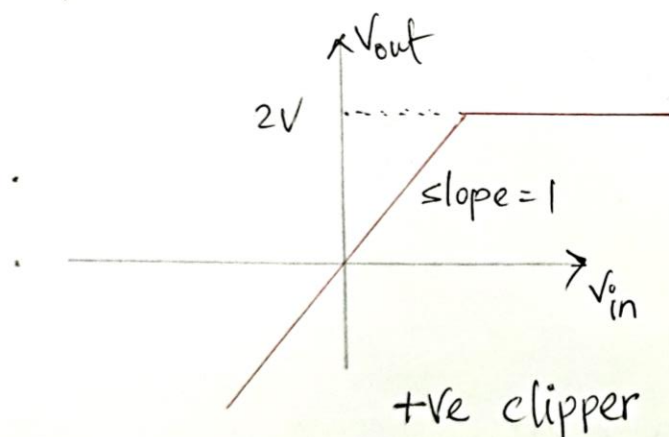

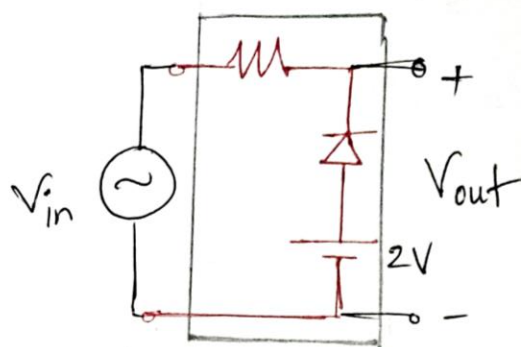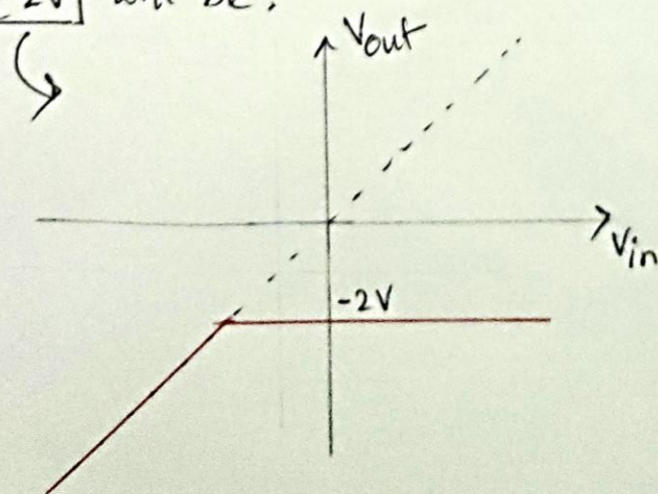
Similarly, VTC of a +ve clipper at $\boxed{-2V}$ will be:




This ckt will pass everything above 2V. And, all voltages below 2V will be clipped at 2V.

$$\text{If } V_{in} < 2V, V_{out} = 2V$$


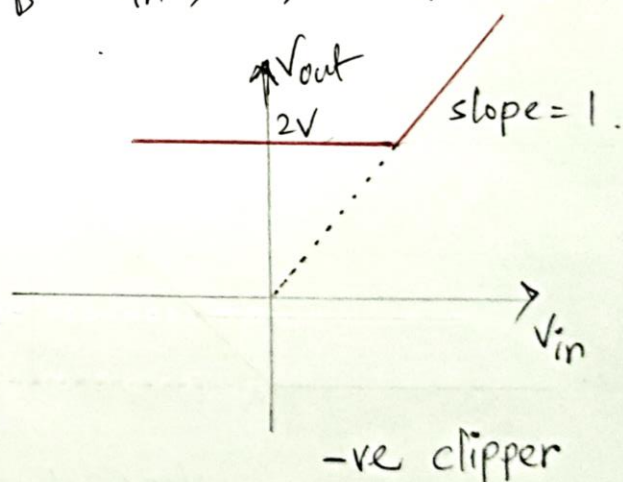
$$\text{If } V_{in} > 2V, V_{out} = V_{in}$$



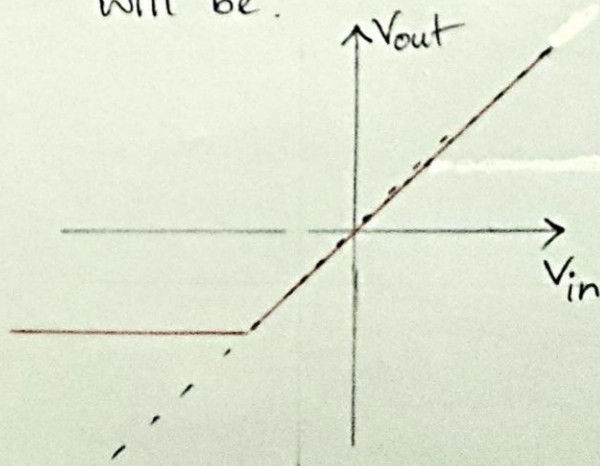And -ve clipper at $\boxed{-2V}$ will be:




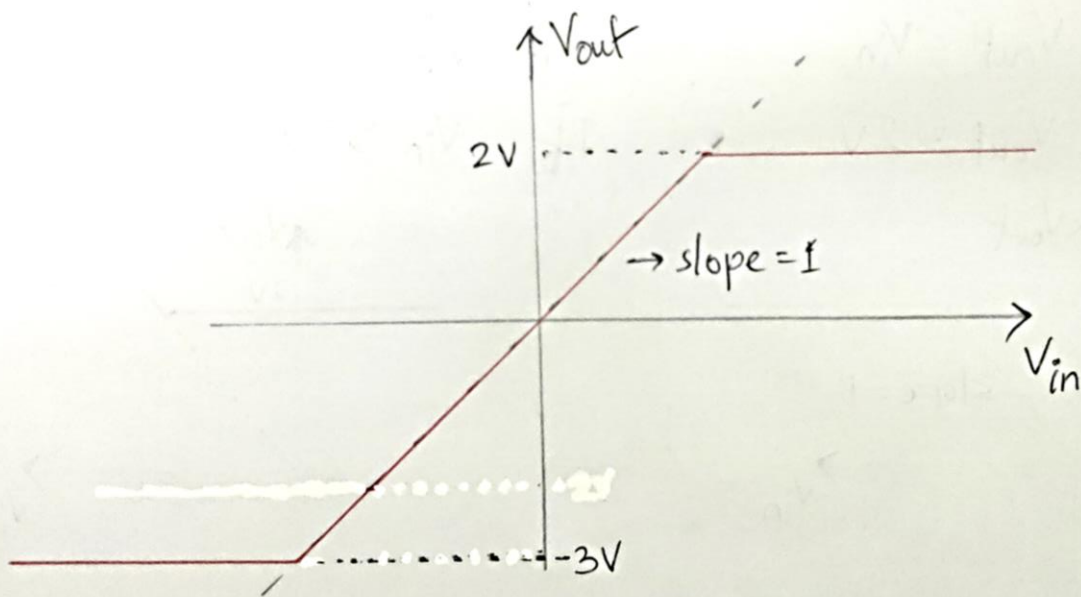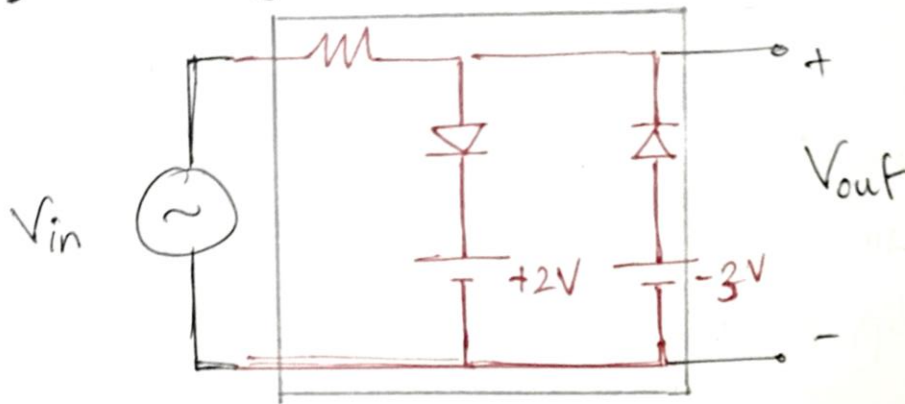If we cascade a +ve clipper at 2V, and, a -ve clipper at -3V, we get,



VTC of a Cascaded Clipper

(5) Voltage Regulator:

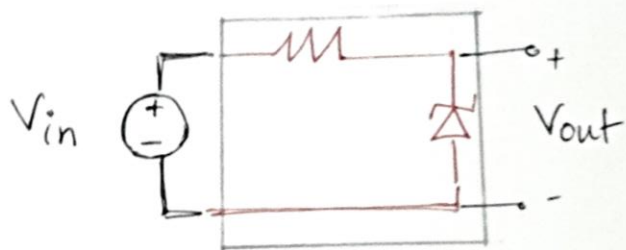


If the zener-diode is ideal, ~~ie~~ the IV of it is completely vertical during breakdown, so, as long as the input is above the breakdown voltage, the zener voltage will be fixed (at the breakdown voltage).

$$\therefore \text{If } V_{in} > V_{breakdown}, \quad V_{out} = V_{breakdown}$$

If the input is below the breakdown voltage, the zener will be open-circuited. So, the output voltage will be equal to the input.


$$\therefore \text{If } V_{in} < V_{breakdown}, \quad V_{out} = V_{in}$$

The VTC looks like this,

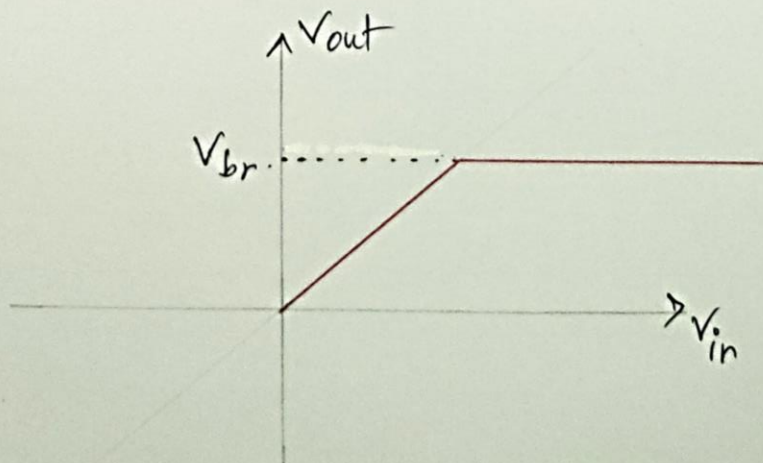


Note the similarity in VTC with that of a clipper circuit.
So, a clipper is kind of like a voltage regulator as well.

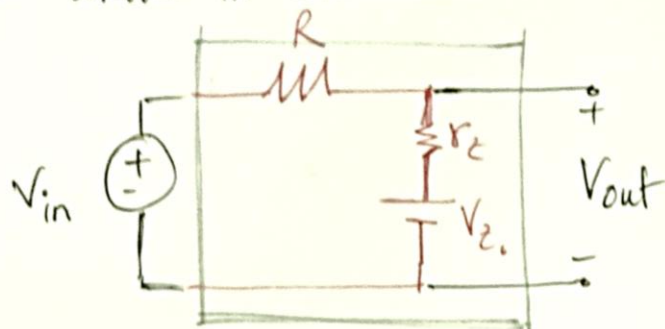If the zener is non-ideal (i.e, there is a slope in the IV characteristics during breakdown), the VTC won't be completely flat. In that case, we have to use the Voltage Source + Series Resistance model of the zener diode while in breakdown.



The VTC will look like this:

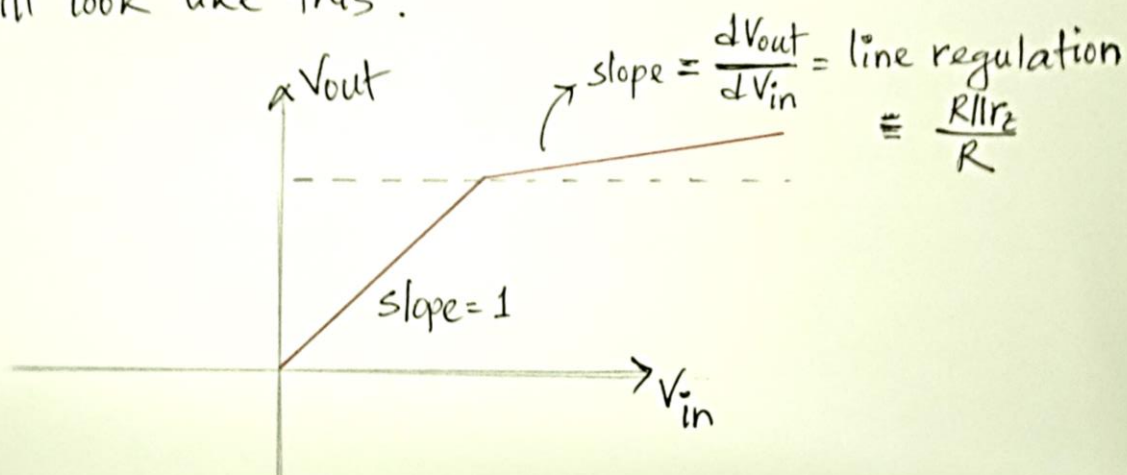

Note that the VTC has a slope in the breakdown region.

The slope is equal to $\frac{dV_{out}}{dV_{in}}$, which is the line-regulation.

So, this is just a graphical representation of the non-ideality of a zener regulator we saw before.