

CSE460 VLSI Design

Final Exam

Date: 8 January, 2022

Time: **05.50 PM - 07.10 PM**

Duration: **1 hour 20 minutes**

PDF preparation & submission: Additional **15 minutes**


Last time to submit: 7.25 PM

Your name, ID, section, slot no. & signature should be at the beginning of your script

This page does not contain any question, the following page does.

Answer any 3 questions. Each question is worth 10 points. Total marks: 3 x 10 = 30.

- Consider an nMOS transistor in a **0.8 μm** process with **$W = 1.2 \mu\text{m}$** and **$L = 0.6 \mu\text{m}$** . In this process, the gate oxide thickness is **100 \AA** and the mobility of electrons is **350 $\text{cm}^2/\text{V}\cdot\text{s}$** . The threshold voltage is **0.7 V**. The permittivity of free space, **$8.85 \times 10^{-14} \text{ F/cm}$** , and the permittivity of SiO_2 is **$k_{\text{ox}} = 3.9$** times as great. [10]
 - Plot I_{ds} vs. V_{ds} for $V_{gs} = 0.5 \text{ V}$ & **3.5 V**. The plot must be properly labeled.
 - Repeat the previous question if the threshold voltage was increased to **4 V**.
- Consider a CMOS inverter in a **0.8 μm** process, where the pMOS transistor is **8 times** wider than the nMOS transistor. Assume a mobility ratio of **2**. [10]
 - What is the beta ratio of the inverter?
 - Draw an approximate DC response curve of the inverter and determine the values of V_{IL} , V_{IH} , V_{OL} & V_{OH} from the DC response curve; such that the noise margins are maximized. (Assume $V_{tn} = |V_{tp}| = 0.2 \text{ V}$; $V_{DD} = 1 \text{ V}$.)
 - Using your answer from Ques. No. 2(b), find the approximate values of NM_H & NM_L and comment on your result.
- A digital system-on-chip in a **1 V, 65 nm** process (with **50 nm** drawn channel lengths and **$\lambda = 25 \text{ nm}$**) has **1 billion** transistors, of which **500 million** are used in type A logic gates and the remainder are used in type B logic gates. The average type **A** transistor width is **12 λ** and the average type **B** transistor width is **8 λ** . A typical behavior of the output signal of both type of logic gates for a single clock cycle is shown below: [10]

 

Assume each transistor contributes **1 fF/ μm** of gate capacitance and **0.8 fF/ μm** of diffusion capacitance. *Neglect* wire capacitance. The system is operating at **1 GHz**.

- Estimate the activity factor for type A & type B logic gates.
 - Estimate the switching power of the system.
- Answer the following questions: [10]
 - Describe the CTS stage of physical design. Why is it required for chip design?
 - Sketch a **3-input NOR** gate with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (**R**). Compute the rising and falling propagation delays of the NOR gate driving **h** identical **NOR** gates using the Elmore delay model. Assume shared diffusion terminal for series transistors, and that every source or drain has fully contacted diffusion.