


Quiz 1 Solution

Tuesday, November 16, 2021 12:23 PM

Slot 1

- Design a CMOS compound gate that implements the following function:
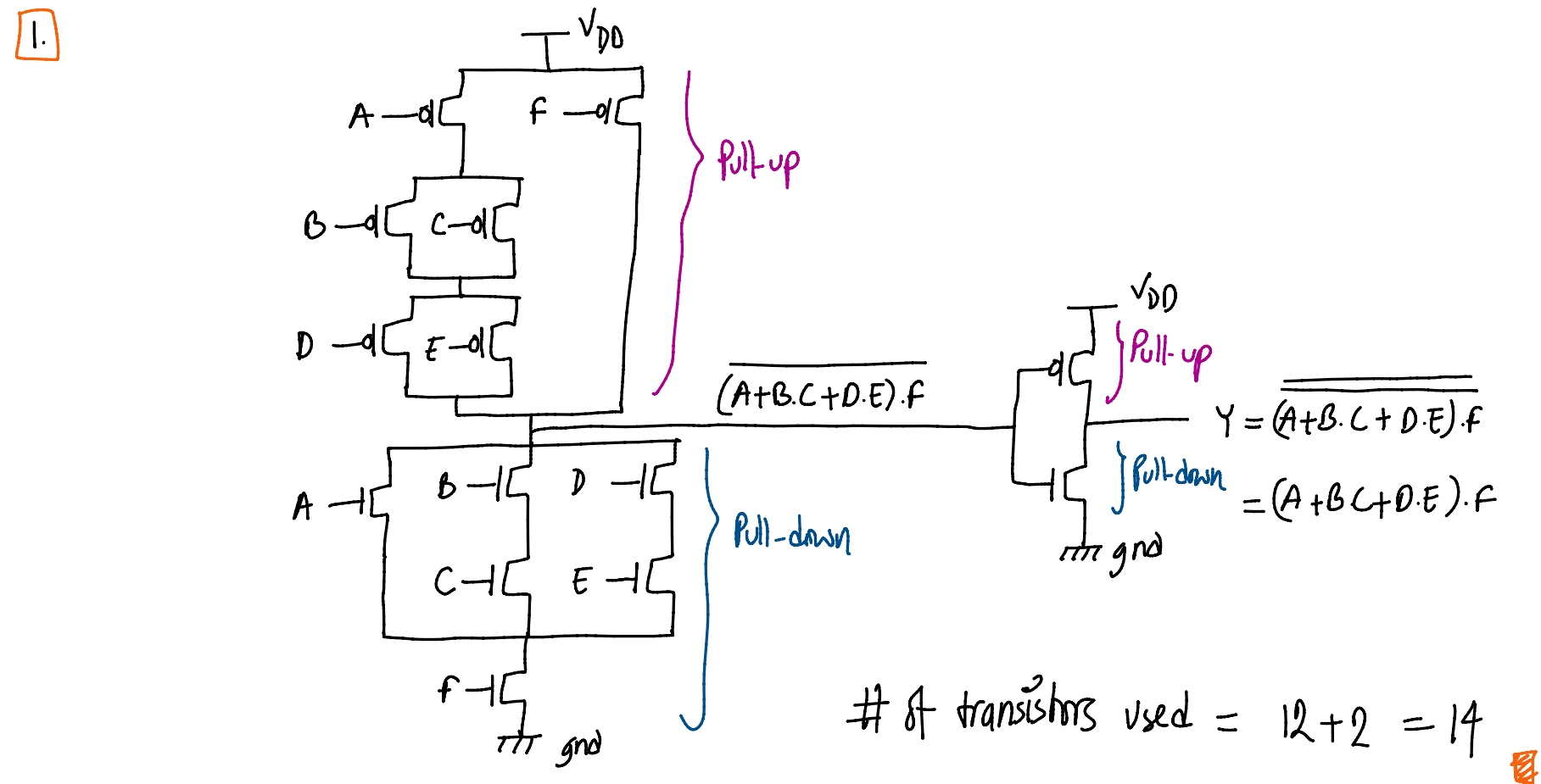
$$Y = (A + B.C + D.E).F$$
 where A, B, C, D, E, F are inputs and Y is the output. Clearly mark the pull-up & pull-down network. How many transistors have you used in your design? [7+2+1]
- Design a positive-edge-triggered D flip-flop using CMOS transmission gates and inverters. Briefly describe how it works. [7+3]




2. Ref: Lecture: 4, slide 17, 18. Textbook: 1.4.9.2 Flip-Flops, Page 17-18

Slot 2

- Design a CMOS compound gate that implements the following function:
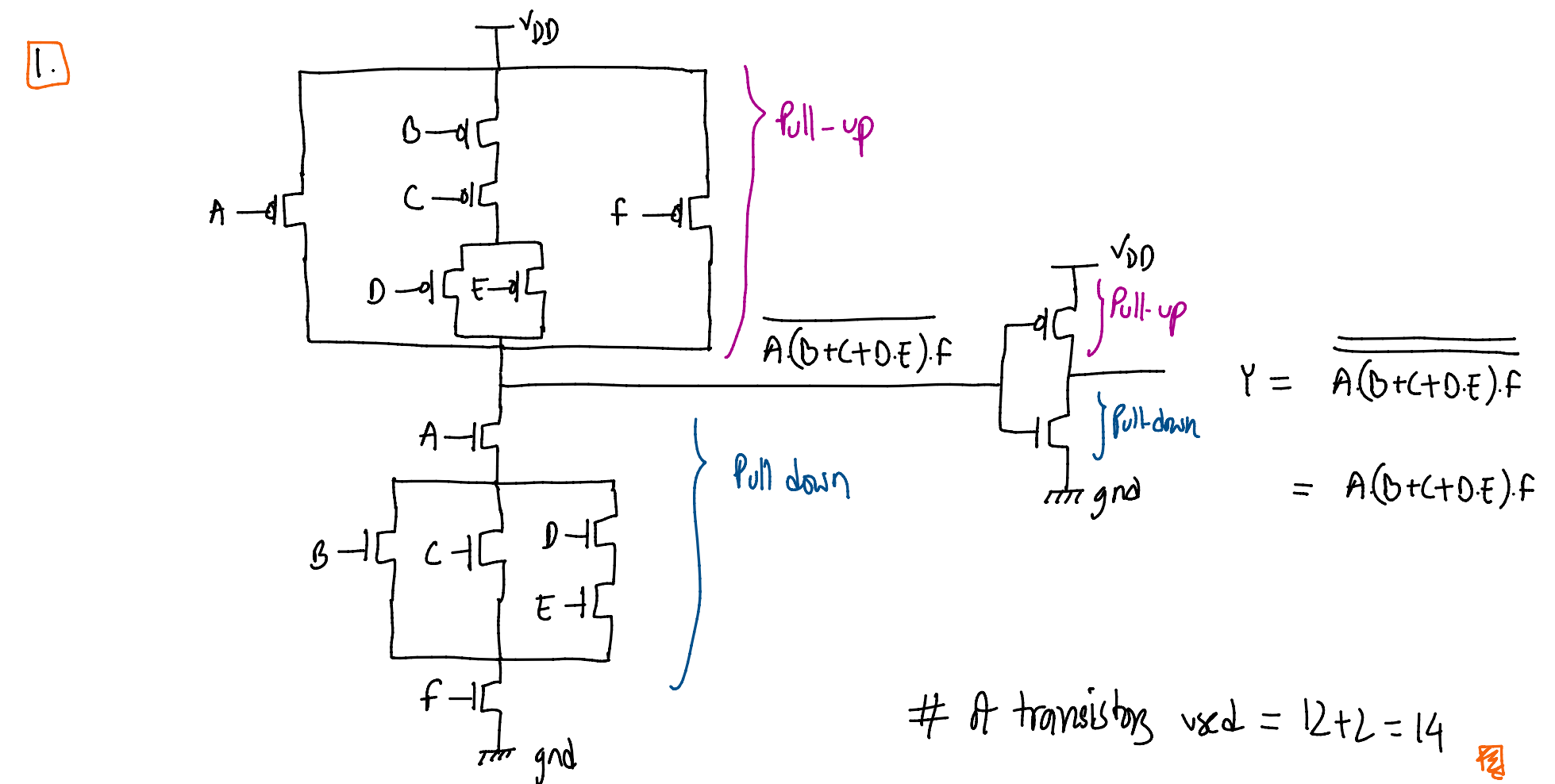
$$Y = A.(B + C + D.E).F$$
 where A, B, C, D, E, F are inputs and Y is the output. Clearly mark the pull-up & pull-down network. How many transistors have you used in your design? [7+2+1]
- Design a complete 4:1 non-inverting MUX using CMOS tristate inverters. Briefly describe how it works. [7+3]



2. Ref: Lecture 4, Slide 12. Textbook: 1.4.8 Multiplexers, Page 15-16.

Makeup

Some useful logic gates are listed below:

Name	Input	Output	Equation
NOT	A	Y	$Y = \bar{A}$
AND	A, B	Y	$Y = A.B$
OR	A, B	Y	$Y = A + B$
XOR	A, B	Y	$Y = A.\bar{B} + \bar{A}.B$
XNOR	A, B	Y	$Y = \bar{A}.\bar{B} + A.B$

- Design a circuit with output **f** and inputs **x1, x0, y1, and y0**. Let **X = x1x0** and **Y = y1y0** represent two 2-digit *binary* numbers. The output **f** should be **1** if the numbers represented by X and Y are equal. Otherwise, **f** should be **0**. You may use the gates from the list above. [10]
- What is a transmission gate? What is a pass transistor? Briefly explain why one is superior to the other in general. [6]
- Describe the current trend in *MOSFET* IC design. [4]

1. Two 2-digit binary numbers : $X (= x_1 x_0)$ & $Y (= y_1 y_0)$

are equal iff $x_1 = y_1$ and $x_0 = y_0$.

Approach 1: $x_1 = y_1 \Rightarrow x_1 = 1 \text{ \& } y_1 = 1 \text{ or, } x_1 = 0 \text{ \& } y_1 = 0$

$$\Rightarrow x_1 y_1 + \bar{x}_1 \bar{y}_1$$

$x_0 = y_0 \Rightarrow x_0 = 1 \text{ \& } y_0 = 1 \text{ or, } x_0 = 0 \text{ \& } y_0 = 0$

$$\Rightarrow x_0 y_0 + \bar{x}_0 \bar{y}_0$$

$$\therefore f = (x_1 y_1 + \bar{x}_1 \bar{y}_1) \cdot (x_0 y_0 + \bar{x}_0 \bar{y}_0)$$

Approach 2: Using the defⁿ of XNOR gates: $A \text{ XNOR } B, A \odot B = \bar{A}.\bar{B} + A.B$

$$f = (x_1 \odot y_1) \cdot (x_0 \odot y_0)$$

Implement the logic function "f" using the logic gates.

2. Ref: lecture 4, slide 3,4. Textbook: 1.4.6 Pass Transistors & Transmission Gates

between these two, transmission gates are superior because it produces both

strong 1 & strong 0; whereas pass transistors can either produce only one of them. 

[3] Ref: lecture 1, Slide 14.

Early MOSFET IC's were built using only PMOS or NMOS. Both PMOS & NMOS processes suffered from poor performance / higher power consumption / yield / reliability.

Current MOSFET IC's are hence built in CMOS technology. 