

# CSE460L: Assignment 1 (Fall 2021)

Sections: 1, 2, 3, 4, 5, 6, 7, 8 & 9

Assignment 1 submission link:

[https://docs.google.com/forms/d/e/1FAIpQLSdBeAsmOK4FBdDCAn0XgES7KuZ\\_JaYTqlb2T5JVVVUb7EE9BA/viewform?usp=sf\\_link](https://docs.google.com/forms/d/e/1FAIpQLSdBeAsmOK4FBdDCAn0XgES7KuZ_JaYTqlb2T5JVVVUb7EE9BA/viewform?usp=sf_link)


Assignment 1 deadline: **9 Nov, 2021, 4.59 PM (BDT)**

## General guidelines

- Assignments are individual
- Each assignment will contain 3 to 4 problems
- **For each problem you will need to prepare 3 parts:**
  1. **Code:** attach a screenshot of your code from Quartus.
  2. **Output: attach \*FULL SCREEN\* screenshots** of
    - Compilation Report - Flow Summary (Compilation report of the .v file)
    - Simulation Report - Simulation Waveforms (Simulation report of the .vwf file)

**[Tampered/edited/cropped screenshots will be considered as a violation of general guidelines and therefore will not be accepted]**

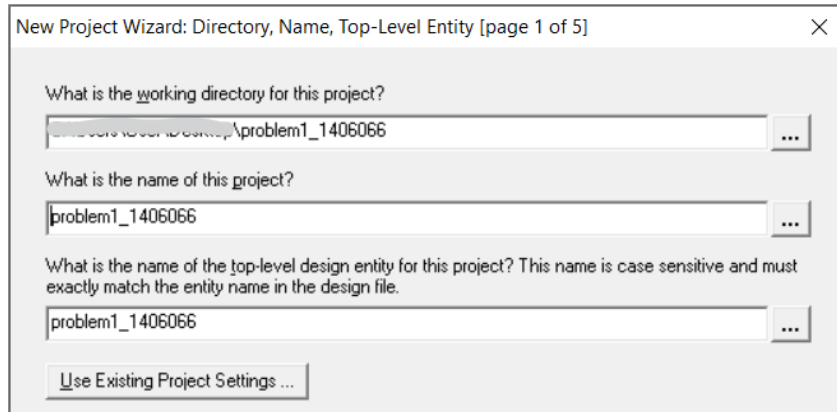3. **Discussion/Explanation:** explain the output waveforms of your simulation report as described in the **Expected Output** section within each problem statement.
- Each problem will be of equal points. You will not be graded on the length/number of code/explanation/outputs; rather on the clarity, readability and precise explanations of your code/logic/outputs
  - Points distribution for each problem is
    - Code: **40%**
    - Output: **20%**
    - Discussion/Explanation of output: **40%**
  - **You will need to create separate directories/project for each problem**
  - **The name of your working directory for each problem of the assignment should be ...\\problem#\_StudentID [# = 1/2/3/4..]**  
For example, for problem 1 the name of the directory should be problem1\_1406066



- Consequently, the name of your main module in the Verilog file should be `problem#_StudentID` [# = 1/2/3/4..]  
Continuing from the previous example, the name of the module should be `problem1_1406066`
- Finally, **compile all the problems for a given assignment into a single pdf file**
- The **name of the pdf should be `Section_StudentID_assignment1.pdf`** (Example: `1_1406066_assignment1.pdf`)

## Problem for Assignment 1

1. Design a logic circuit in Verilog that will take one **3-bit** input **A**, check whether all of the input bits are **equal or not** and determine the **logic level (0/1)** of the unique bit. Find the possible input conditions and the expected outputs in the following table: **[15]**

Possible input condition	Output
All bits are equal	3
Unique bit at position 2	2
Unique bit at position 1	1
Unique bit at position 0	0

### Expected Output:

Show all possible outputs in your timing diagram with appropriate inputs and briefly explain your results.

2. Design a **5-bit end around left shift register** that operates at the **negative edge** of a clock in Verilog with external **load** functionality. For example, the output of the shift register would be ( for each **negedge** clock time  $t(i)$  to  $t(i+2)$  and so on): **[15]**

$t(i)$	$t(i+1)$	$t(i+2)$
10110	01101	11010

### Expected Output:

Perform the simulation for enough time to get at least **two** repetitions of the initial input after the external **load**. Determine the total number of clock cycles required to get one repetition of the input from the timing diagram and briefly explain your reasoning for that.